

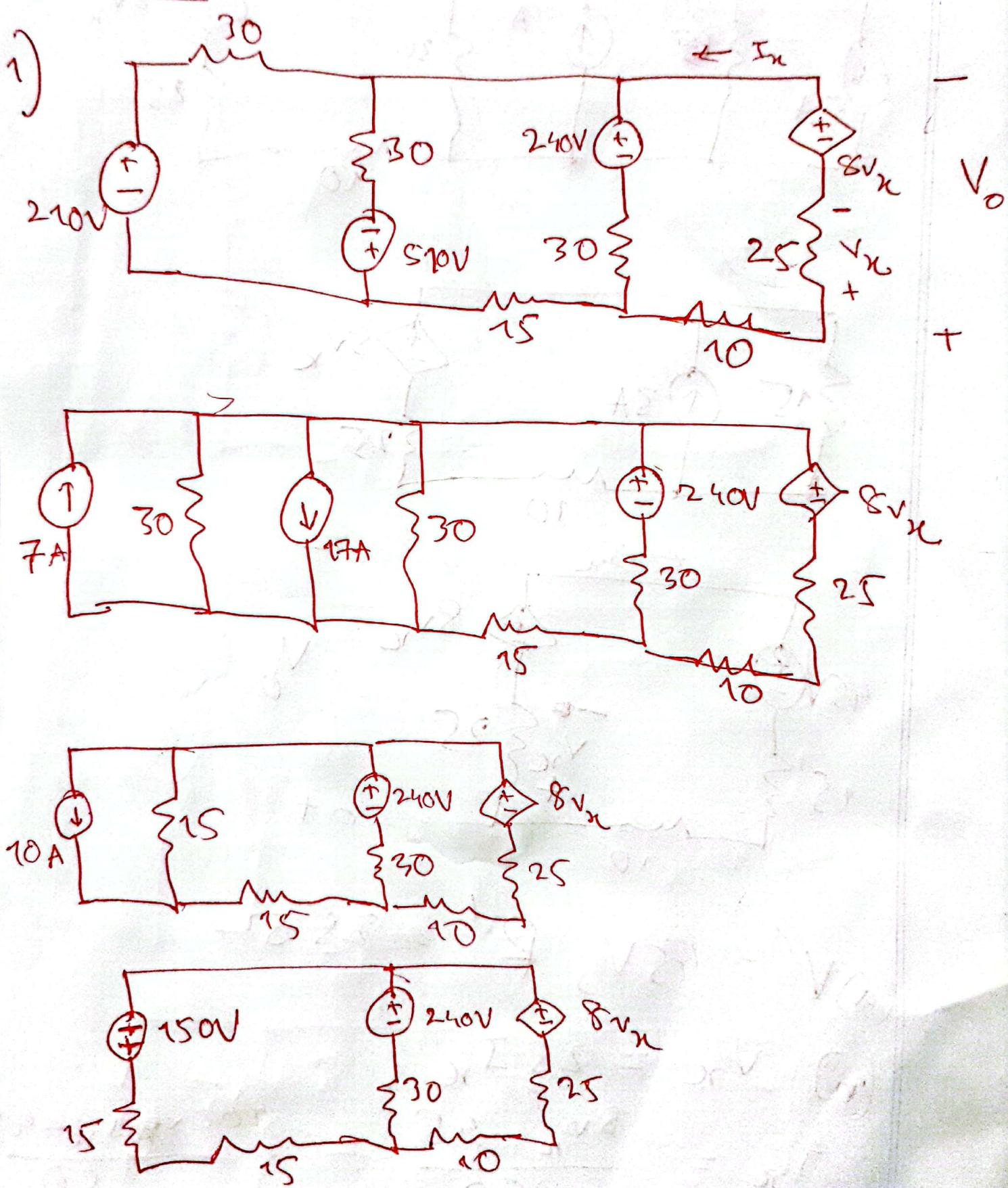
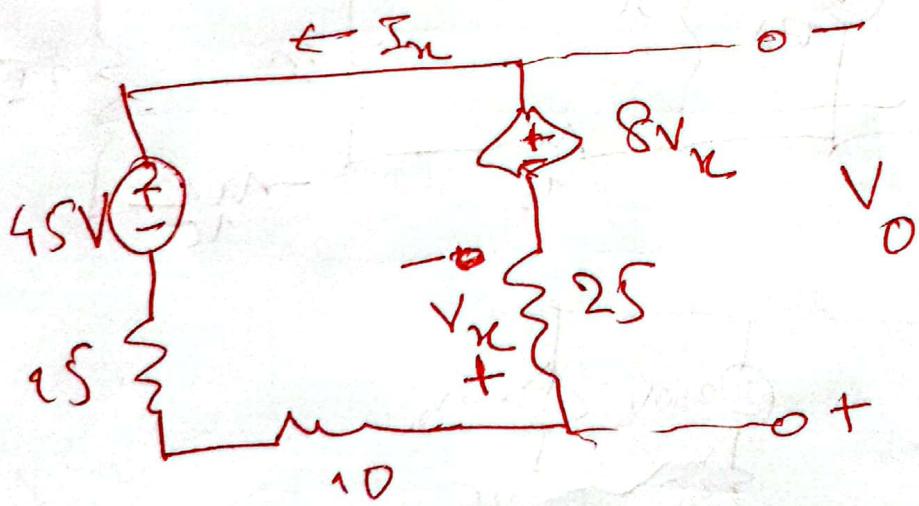


Set - A

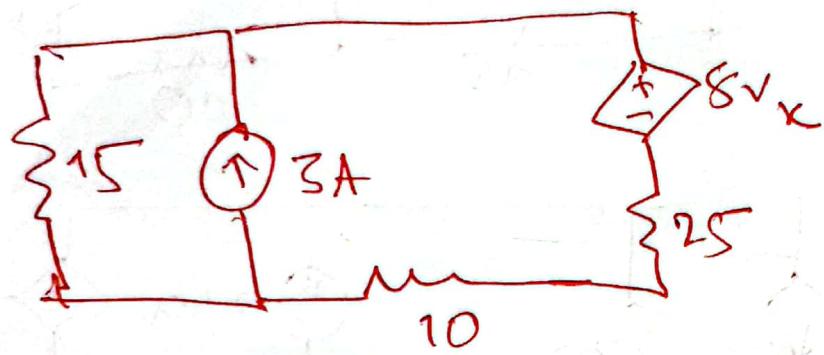

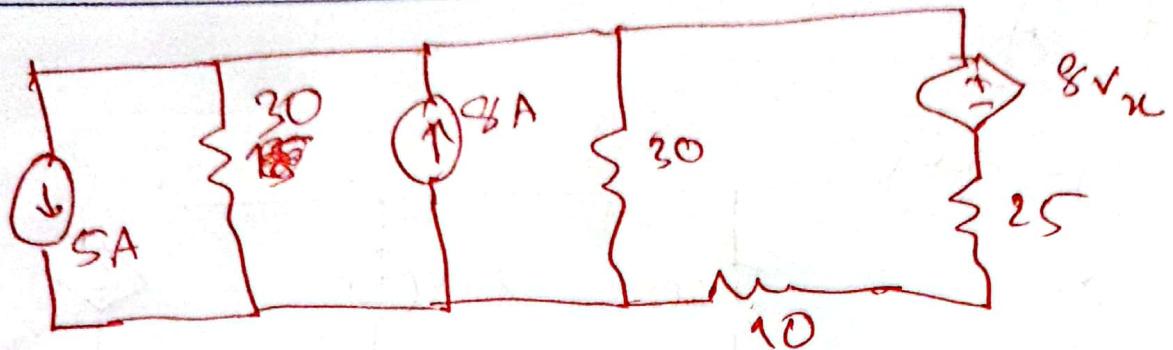

$$(a) V' = 45V, R' = 25\Omega$$

$$(b) V_n = 2.5 I_n$$

$$I_n = \frac{8V_n - 45}{50} = \frac{200 - 8V_n - 45}{50}$$

$$\text{or, } i_n = 4i_n - \frac{45}{50}$$

$$\text{or, } i_x = \frac{45}{50} \cdot \frac{1}{3} = 0.3A$$




$$v_x = 7.5V$$



$$(c) \cancel{8v_n} - v_o + v_x - 8v_n = 0$$


$$\text{or, } v_o = -7v_x = -52.5V$$

Set - B

1) +

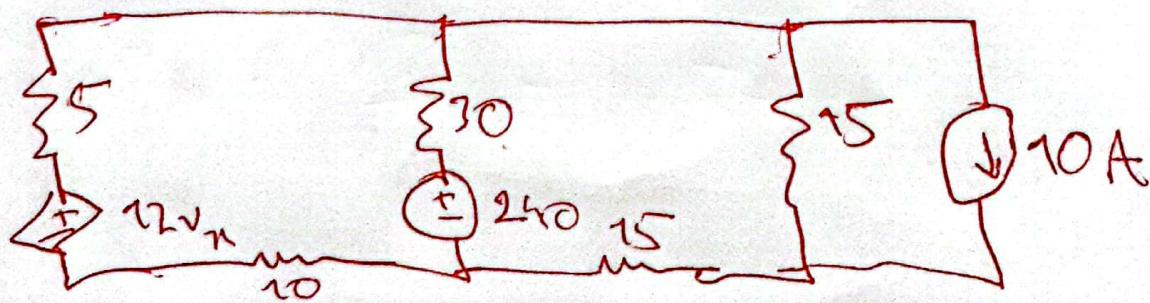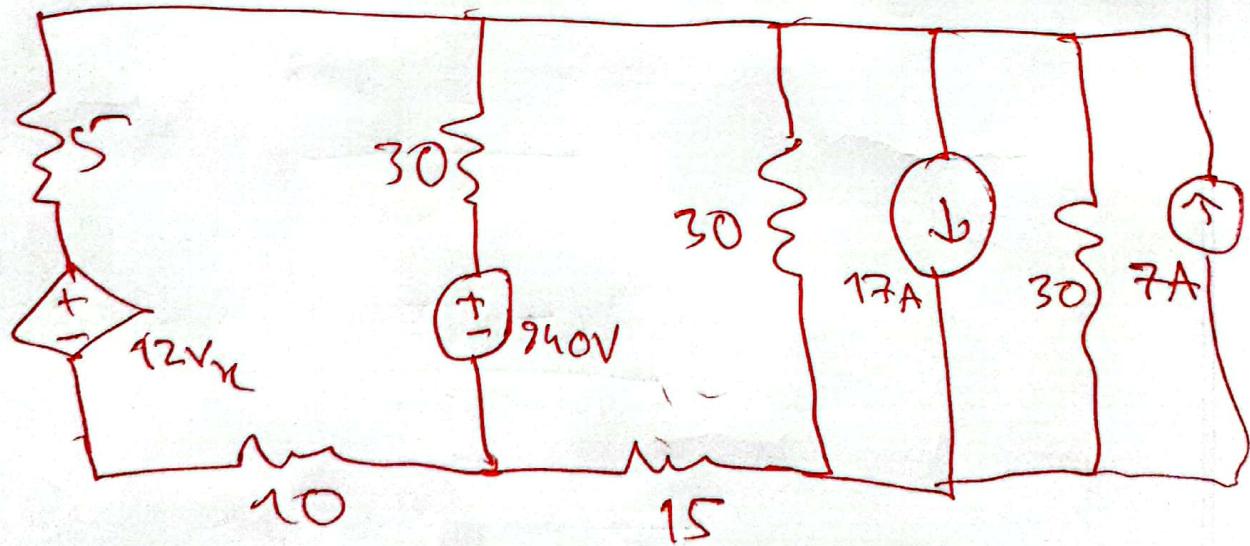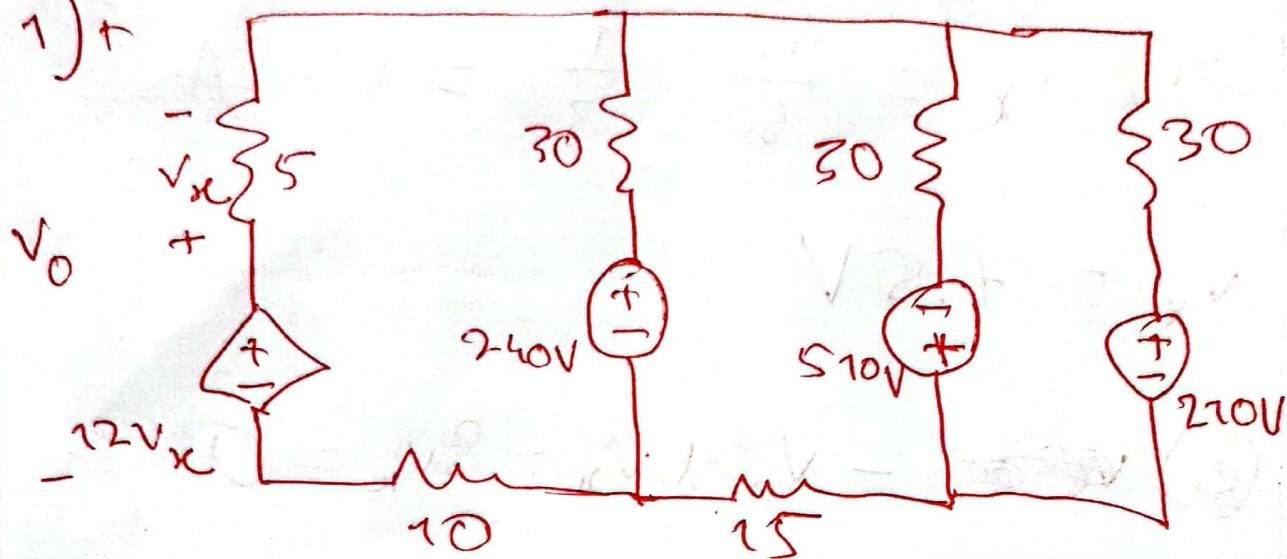

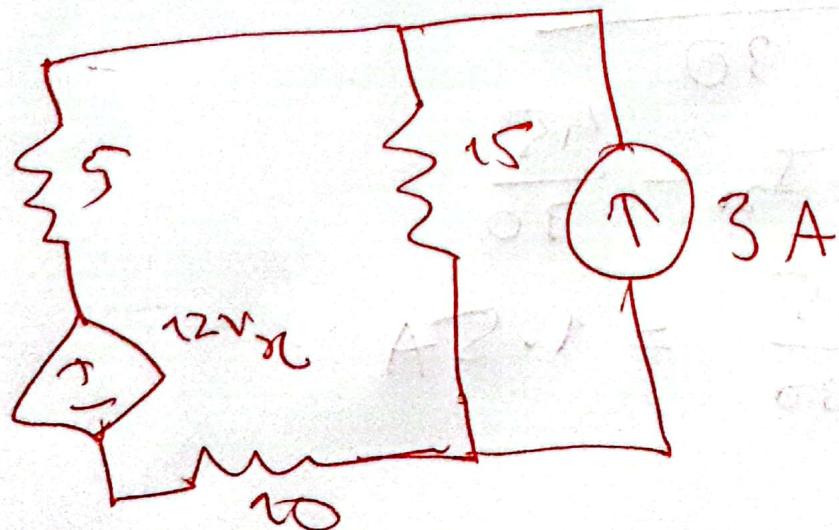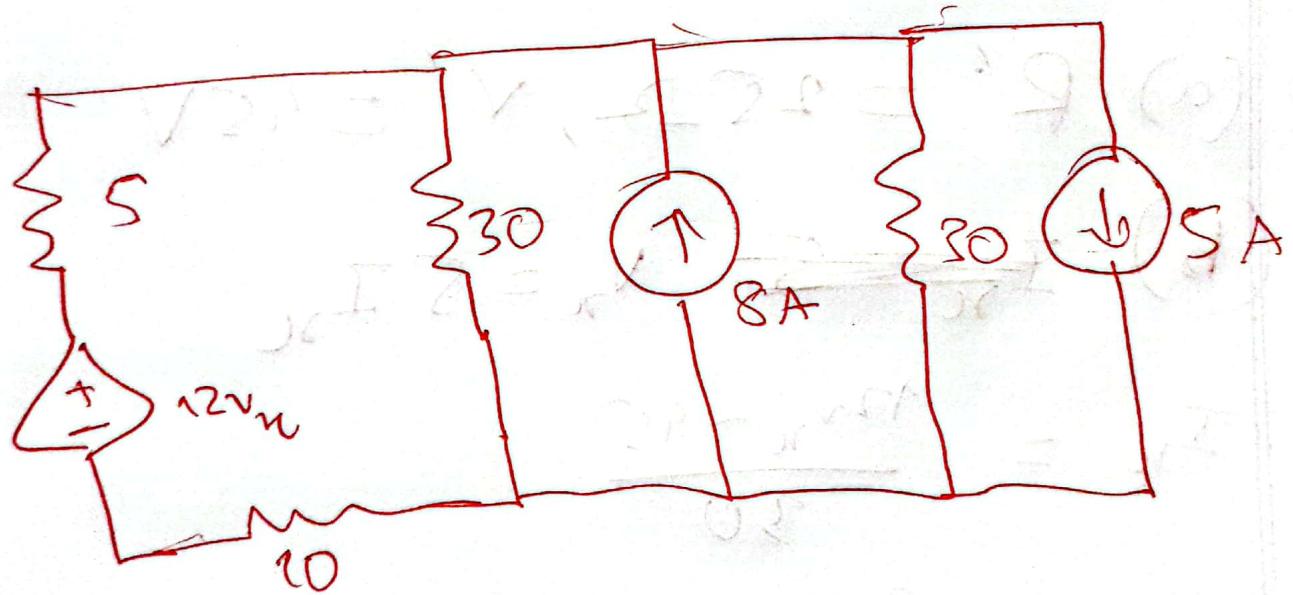

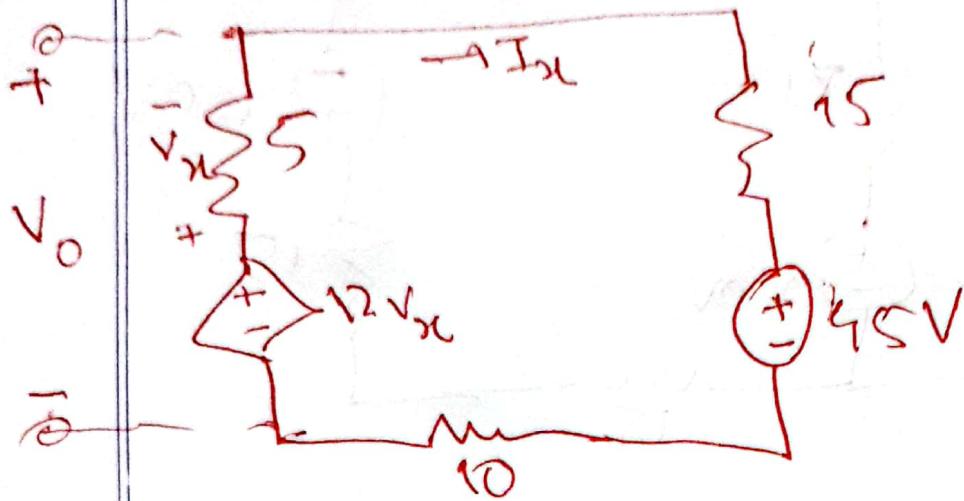

$$(a) R' = 25\ \Omega, V' = 45V$$

$$(b) \cancel{I_x} \quad V_x = 5 I_x$$

$$I_x = \frac{12V - 45}{30}$$

$$= \frac{60 I_x - 45}{30}$$

$$= 2 I_x - \frac{45}{30}$$


$$\text{or, } I_x = \frac{45}{30} = 1.5A$$

$$V_n = 5I_n = 7.5V$$

$$(c) -V_o - V_n + 12V_n = 0$$

$$\text{or, } V_o = 11V_n = 82.5V$$

Q.

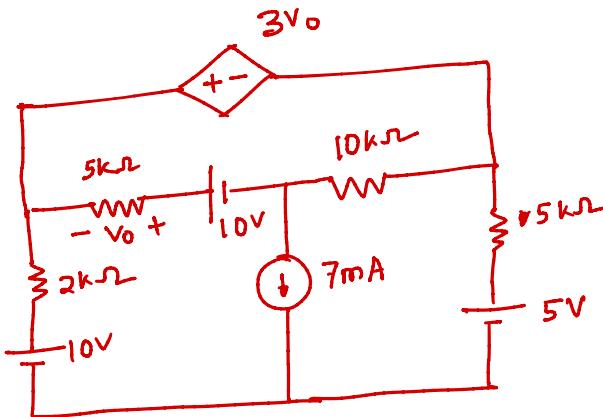


- (a) Use Nodal/Mesh analysis to find out the node voltage / mesh currents
- (b) Find out the voltage and power across dependent source.

Mesh analysis

Supermesh
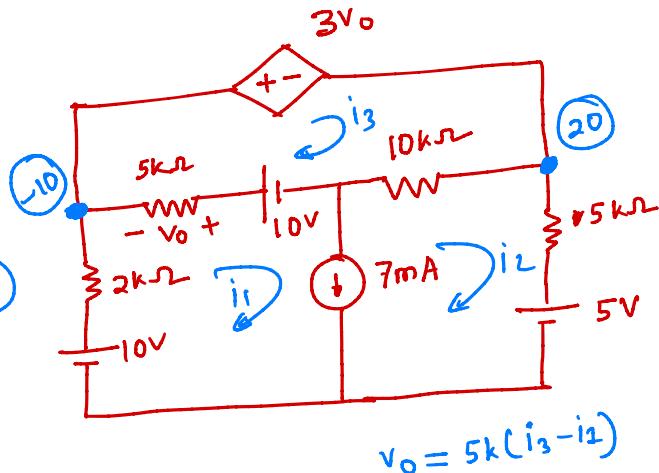
$$\begin{aligned}
 & -10 + 2k i_1 + 5k(i_1 - i_3) + 10 \\
 & + 10k(i_2 - i_3) + 5k i_2 + 5 = 0 \\
 \Rightarrow & 7ki_1 + 15ki_2 - 15ki_3 = -5 - i \quad (i) \\
 i_1 - i_2 = & 7\text{mA} \quad (ii)
 \end{aligned}$$



mesh-3

$$\begin{aligned}
 & 10k(i_3 - i_2) - 10 + 5k(i_3 - i_1) + 3V_0 = 0 \\
 & 10k(i_3 - i_2) - 10 + 5k(i_3 - i) + 15k(i_3 - i_1) = 0 \\
 \Rightarrow & 10k(i_3 - i_2) + 20k(i_3 - i_1) = 10 \\
 \Rightarrow & 10k(i_3 - i_2) + 20k(i_3 - i) = 10 \\
 \Rightarrow & -20ki_1 - 10ki_2 + 30ki_3 = 10 \\
 \Rightarrow & -2ki_1 - ki_2 + 3ki_3 = 1 \quad (iii) \\
 i_1 = & 10\text{mA} \quad i_2 = 3\text{mA} \quad i_3 = 8\text{mA}
 \end{aligned}$$

voltage across dependent source $\pm 30V$

current = 8mA

$$\begin{aligned}
 \text{Sup power} = +ri = & +(-30)(8 \times 10^{-3}) \\
 = & -0.24\text{watt} \quad (\text{Ans})
 \end{aligned}$$

Nodal analysis

Supernode


$$v_1 - v_3 = 3v_0$$

$$v_0 = v_2 + 10 - v_1$$

$$\Rightarrow v_1 - v_3 = 3(v_2 + 10 - v_1)$$

$$\Rightarrow v_1 - v_3 = 3v_2 + 30 - 3v_1$$
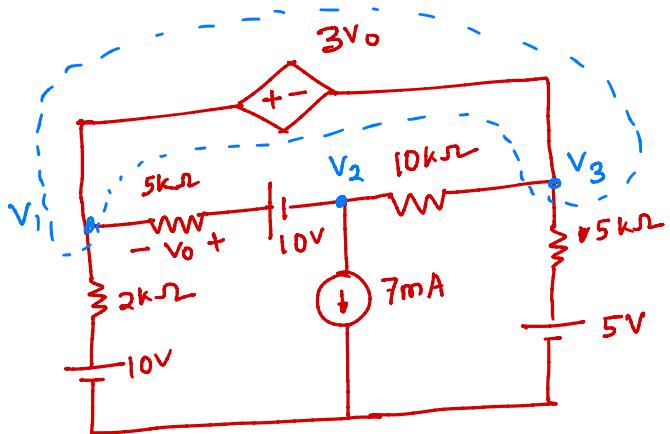
$$\Rightarrow 4v_1 - 3v_2 - v_3 = 30 \quad \textcircled{i}$$



KCL at supernode

$$\frac{v_1 - 10}{2k} + \frac{v_1 - (v_2 + 10)}{5k} + \frac{v_3 - 5}{5k} = \frac{v_2 - v_3}{10k}$$

$$\Rightarrow 5(v_1 - 10) + 2v_1 - 2(v_2 + 10) + 2(v_3 - 5) = v_2 - v_3$$

$$\Rightarrow 7v_1 - 3v_2 + 3v_3 - 50 - 20 - 10 = 0$$

$$\Rightarrow 7v_1 - 3v_2 + 3v_3 = 80 \quad \textcircled{ii}$$

$$\begin{aligned} v_1 &= -10 \text{ V} \\ v_2 &= -30 \text{ V} \\ v_3 &= 20 \text{ V} \end{aligned}$$

KCL at node 2

$$\frac{v_1 - (v_2 + 10)}{5k} = 7\text{mA} + \frac{v_2 - v_3}{10k}$$

$$\Rightarrow 2v_1 - 2(v_2 + 10) = 70 + v_2 - v_3$$

$$\Rightarrow 2v_1 - 3v_2 + v_3 = 90 \quad \textcircled{iii}$$


voltage across
dependent source $\pm 30 \text{ V}$

$$\begin{aligned} \text{power} &= +v_1^i \\ &= -0.24 \text{ watt} \end{aligned}$$

Done < > AA

(c) [3 marks] Determine the value of V_o .

■ Question 2 of 4 [CO3] [15 marks]

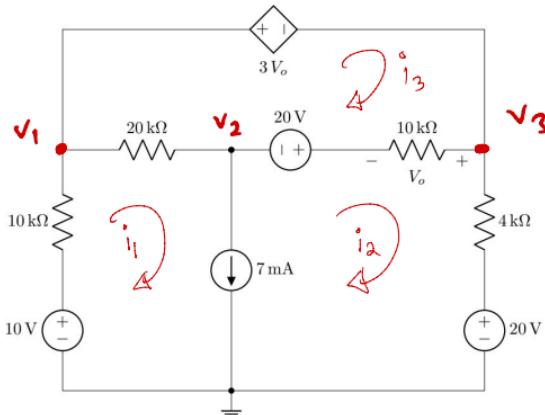

Apply Nodal/Mesh analysis to answer the following questions-

- (a) [12 marks] Find all the node voltages/mesh currents in the circuit shown above. Note that, depending on the analysis method you are applying, you have to determine either the mesh currents or the node voltages, not both.

[A hint: derive all the equations at first, as correct formation of the nodal/mesh equations bear majority of the marks. Proceed to solve then.]

- (b) [3 marks] Determine the power of the $3V_o$ dependent voltage source (with appropriate \pm sign). Also mention, whether the source is supplying or consuming the power.

■ Question 3 of 4 [CO3] [15 marks]

Supermesh

$$-10 + 10k i_1 + 20k(i_1 - i_3) - 20 + 10k(i_2 - i_3) + 4k i_2 + 20 = 0$$

$$\Rightarrow 30k i_1 + 14k i_2 - 30k i_3 = 10 \quad \text{---} \textcircled{i}$$

$$i_1 - i_2 = 7 \times 10^{-3} \quad \text{---} \textcircled{ii}$$

$$v_o = 10k(i_3 - i_2)$$

mesh-3

$$10k(i_3 - i_2) + 20 + 20k(i_3 - i_1) + 3v_o = 0$$

$$\Rightarrow 10k(i_3 - i_2) + 20 + 20k(i_3 - i_1) + 30k(i_3 - i_2) = 0$$

$$\Rightarrow -20k i_1 - 40k i_2 + 60k i_3 = -20 \quad \text{---} \textcircled{iii}$$

$$i_1 = -3 \text{mA} \quad i_2 = -10 \text{mA} \quad i_3 = -8 \text{mA}$$

dependent source power

$$v_1 = (3 \text{mA} \times 10 \text{k}\Omega) + 10 = 40 \text{V}$$

$$v_2 = (-10 \text{mA} \times 4 \text{k}\Omega) + 20 = -20$$

$$\text{voltage across the source} = 60 \text{V}$$

$$\begin{aligned} P &= +vi = 60(-8 \text{mA}) \\ &= -0.48 \text{Watt} \\ &\quad (\text{Ans.}) \end{aligned}$$

Nodal analysis

Supernode

$$\frac{v_1 - 10}{10} + \frac{v_1 - v_2}{20} + \frac{v_3 - 20}{4} = \frac{(v_2 + 20) - v_3}{10}$$

$$\Rightarrow \underline{2v_1 - 20 + v_1 - v_2 + 5v_3 - 100} = \underline{2v_2 + 40 - 2v_3}$$

$$\Rightarrow 3v_1 - 3v_2 + 7v_3 = 160 \quad \textcircled{i}$$

$$v_1 - v_3 = 3v_0$$

$$\Rightarrow v_1 - v_3 = 3(v_3 - (v_2 + 20))$$

$$\Rightarrow v_1 - v_3 = 3v_3 - 3v_2 - 60$$

$$\Rightarrow v_1 + 3v_2 - 4v_3 = -60 \quad \textcircled{ii}$$

node 2: $\frac{v_1 - v_2}{20} = 7 + \frac{(v_2 + 20) - v_3}{10}$

$$\Rightarrow v_1 - v_2 = 140 + 2v_2 + 40 - 2v_3$$

$$\Rightarrow v_1 - 3v_2 + 2v_3 = 180 \quad \textcircled{iii}$$

$$v_1 = 40V \quad v_2 = -60V \quad v_3 = -20V$$

$$\text{voltage across source} = 40 - (-20) = 60V$$

current entering through the +ve terminal

$$\frac{v_1 - 10}{10} + \frac{v_1 - v_2}{20} \Rightarrow +^{\circ}x = 0$$


$$i_x = -8mA$$

$$\therefore \text{power} = +vi = 60 (-8mA)$$

$$= -0.48W$$

Main Set-A (Q-3)

Mesh Analysis:

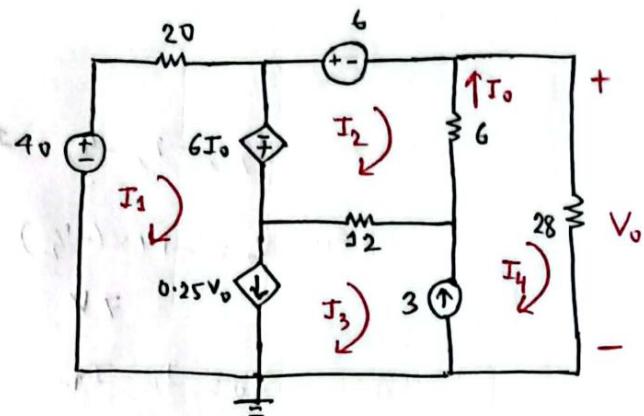

$$I_0 = I_4 - I_2$$

$$V_0 = 28I_4$$

Supermesh KCL: $I_1 - I_3 = 0.25 \times (28I_4)$

$$\Rightarrow I_1 - I_3 - 7I_4 = 0 \quad \dots (1)$$


$$I_4 - I_3 = 3 \quad \dots (2)$$

Supermesh KVL:

$$20I_1 - 6(I_4 - I_2) + 12(I_3 - I_2) + 6(I_4 - I_2) + 28I_4 = 40$$

$$\Rightarrow 20I_1 - 12I_2 + 12I_3 + 28I_4 = 40 \quad \dots (3)$$

Nodal Analysis

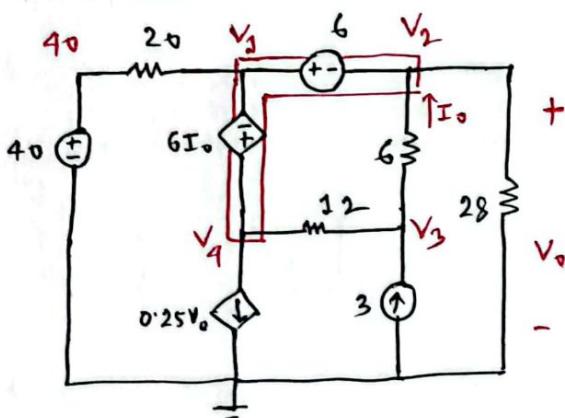

$$V_0 = V_2$$

$$I_0 = \frac{V_3 - V_2}{6}$$

(b)

$V_0 = V_2 = 14V$
$I_0 = \frac{35 - 14}{6} = 3.5A$

Mesh-2 KVL

$$6 + 6(I_2 - I_4) + 12(I_2 - I_3) + 6(I_4 - I_2) = 0$$

$$\Rightarrow 12I_2 - 12I_3 = -6 \quad \dots (4)$$

Solving (1), (2), (3), (4)

$$I_1 = 1A$$

$$I_2 = -3A$$

$$I_3 = -2.5A$$

$$I_4 = 0.5A$$

(b)

$$I_0 = 0.5 + 3 = 3.5A$$

$$V_0 = 28 \times 0.5 = 14V$$

Supernode KVL: $V_1 - V_2 = 6 \quad \dots (1)$

$$V_4 - V_1 = 6I_0 = 6 \times \frac{V_3 - V_2}{6}$$

$$\Rightarrow V_1 - V_2 + V_3 - V_4 = 0 \quad \dots (2)$$

Supernode KCL:

$$\frac{V_2}{28} + \frac{V_2 - V_3}{6} + \frac{V_3 - 40}{20} + \frac{V_4 - V_3}{12} + 0.25V_2 = 0$$

$$\Rightarrow \frac{V_3}{20} + \frac{19V_2}{42} - \frac{V_3}{4} + \frac{V_1}{12} = 2 \quad \dots (3)$$

KCL at Node-3: $\frac{V_3 - V_2}{6} + \frac{V_3 - V_4}{12} = 3$


$$\Rightarrow -\frac{V_2}{6} + \frac{V_3}{4} - \frac{V_4}{12} = 3 \quad \dots (4)$$

Solving (1), (2), (3), (4)

$$V_3 = 20V, V_2 = 14V, V_3 = 35V, V_4 = 91V$$

Main Set - B (Q-3)

Mesh Analysis:

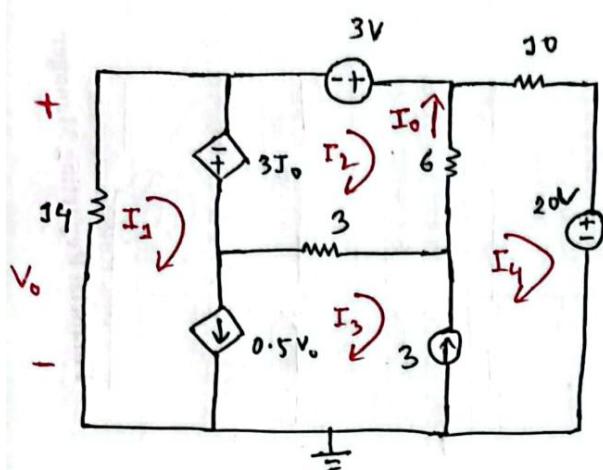

$$V_0 = -14I_1 \quad I_0 = I_4 - I_2$$

Supermesh KCL: $I_4 - I_3 = 3 \dots (1)$

$$I_3 - I_2 = 0.5V_0 = 0.5(-14I_1)$$

$$\Rightarrow 8I_1 - I_3 = 0 \dots (2)$$

Supernode KVL:

$$14I_1 - 3(I_4 - I_2) + 3(I_3 - I_2) \\ + 6(I_4 - I_2) + 10I_4 + 20 = 0$$

$$\Rightarrow 14I_1 - 6I_2 + 3I_3 + 13I_4 = -20 \dots (3)$$

Mesh-2 KVL: $-3 + 6(I_2 - I_4) + 3(I_2 - I_3) \\ + 3(I_4 - I_2) = 0$

$$6I_2 - 3I_3 - 3I_4 = 3 \dots (4)$$


Solving (1), (2), (3), (4)

$$I_1 = -0.5A, I_2 = -2A, I_3 = -4A, I_4 = -1A$$

(b) $V_0 = -14(-0.5) = 7V$

$$I_0 = -1 - (-2) = 1A$$

Nodal Analysis:

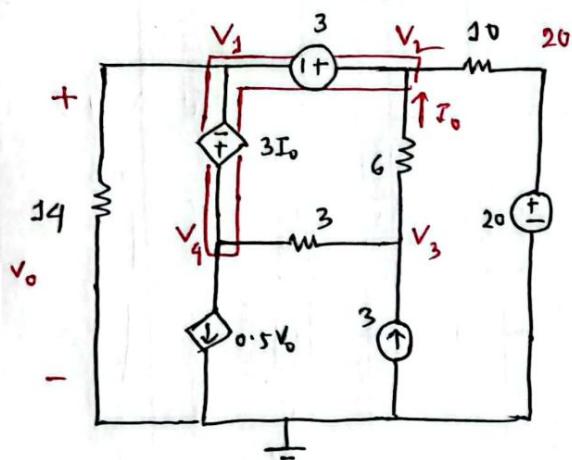

$$V_0 = V_1 \quad I_0 = \frac{V_3 - V_2}{6}$$

(b) $V_0 = V_3 = 7V$

$$I_0 = \frac{16 - 10}{6} = 1A$$

Supernode KVL: $V_2 - V_1 = 3 \dots (1)$

$$V_4 - V_3 = 3I_0 = 3 \times \frac{V_3 - V_2}{6}$$

$$\Rightarrow V_1 - \frac{V_2}{2} + \frac{V_3}{2} - V_4 = 0 \dots (2)$$

Supernode KCL:

$$\frac{V_2 - 20}{20} + \frac{V_2 - V_3}{6} + \frac{V_1}{14} + \frac{V_4 - V_3}{3} + 0.5V_3 = 0$$

$$\Rightarrow \frac{4V_3}{7} + \frac{4V_2}{15} + \left(-\frac{V_3}{2}\right) + \frac{V_4}{3} = 2 \dots (3)$$


Node-3 KCL: $\frac{V_3 - V_4}{3} + \frac{V_3 - V_2}{6} = 3$

$$\Rightarrow -\frac{V_2}{6} + \frac{V_3}{2} - \frac{V_4}{3} = 3 \dots (4)$$

Solving (1), (2), (3), (4)

$$V_3 = 7V, V_2 = 10V, V_3 = 16V, V_4 = 10V$$

4. @ Set - 1

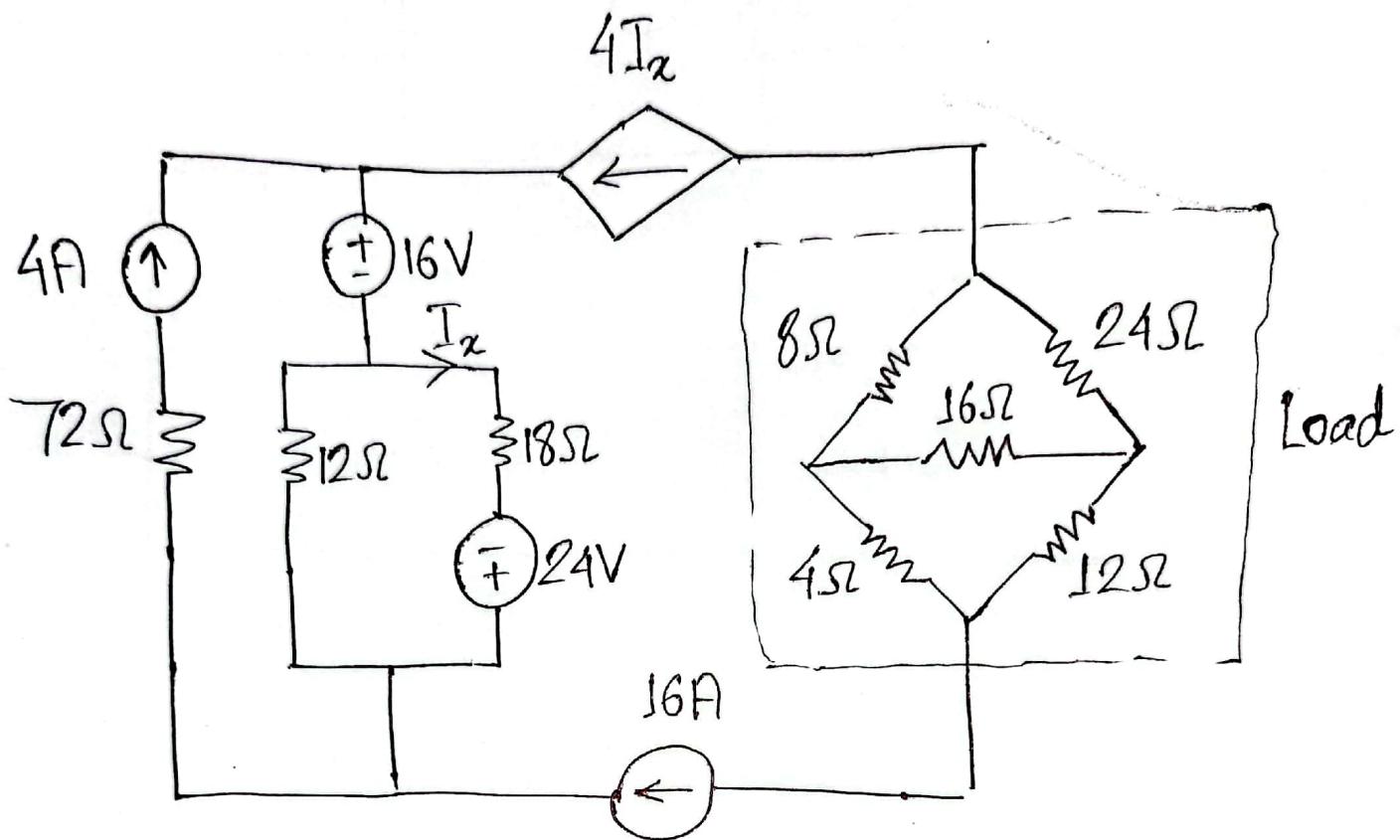


Q. In this circuit, find the value of I_x

$\Rightarrow 4I_x$ is in series with 16A.

$$\therefore -4I_x = 16 \text{ [considering current direction]}$$

$$\Rightarrow I_x = -4A$$

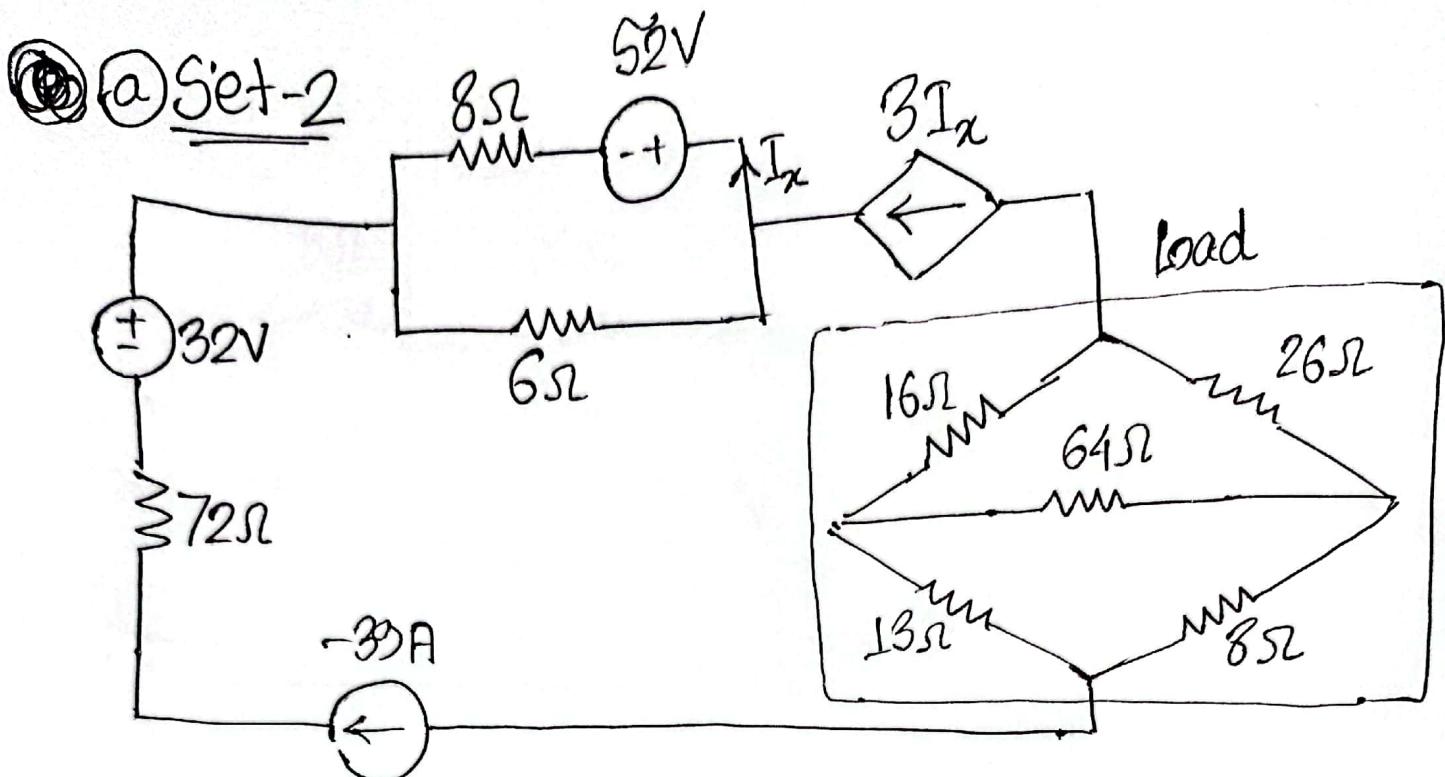


In the circuit find I_x .

In the circuit $3I_x$ is in series with $-39A$.


Hence, $3I_x = 39$ [considering current direction]

$$\Rightarrow I_x = 13A$$


4(b) Set-1

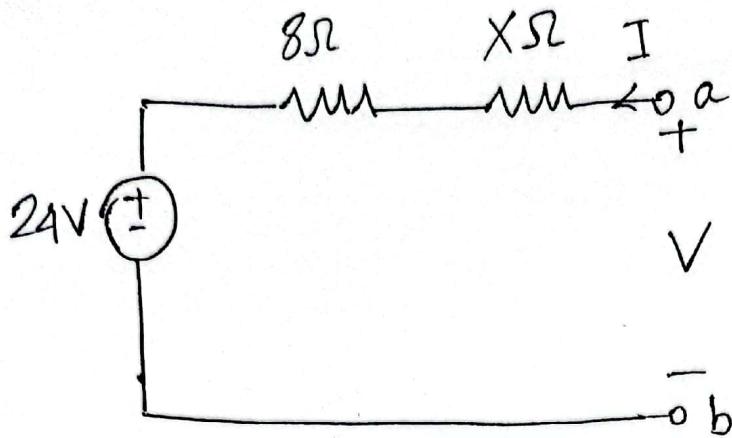

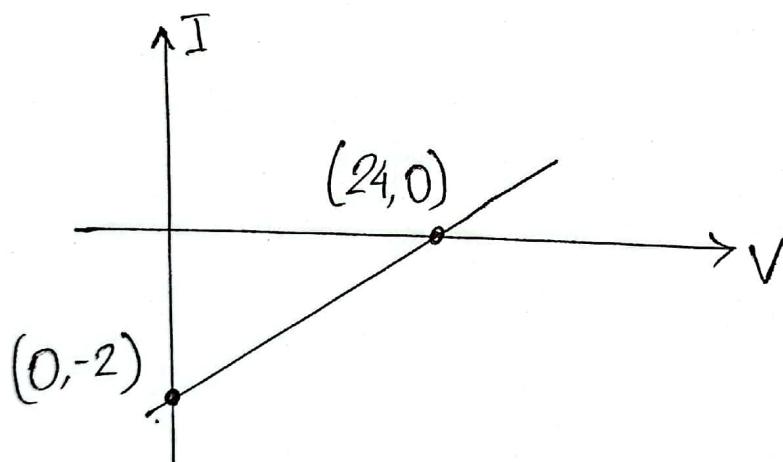If the current, I vs. voltage V has the following relationship, determine the value of X .



At point $(0, -2)$, the ckt becomes

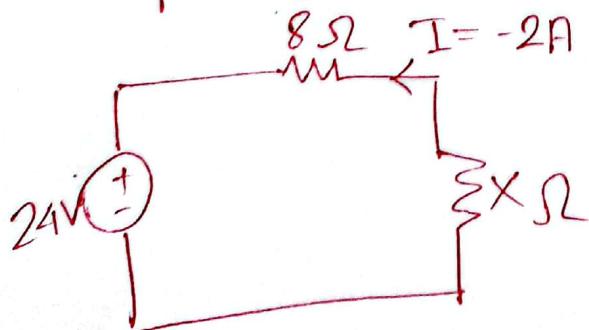


$$\text{So, } \frac{-24}{8+X} = -2$$


$$\Rightarrow 24 = 16 + 2x$$

$$\Rightarrow X = 8/2 = 4$$


⑥ Set I_2 (proposed)

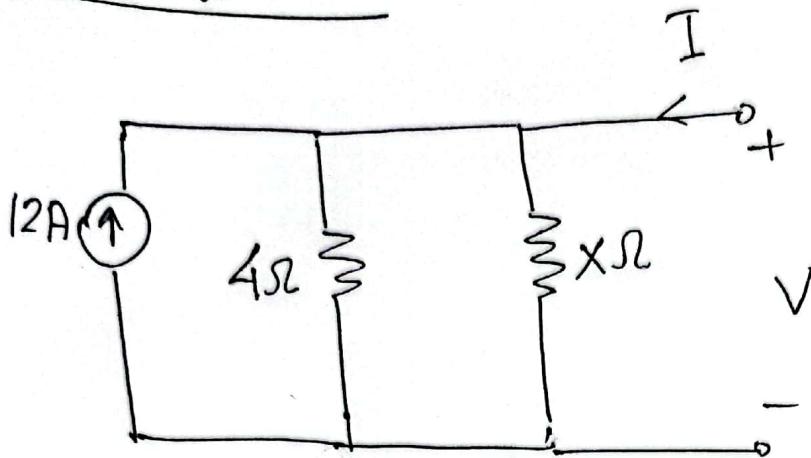

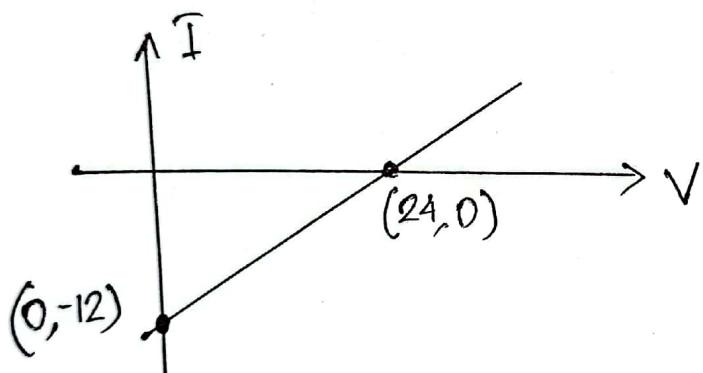If the current, I vs voltage, V has the following relationship, determine the value of x .



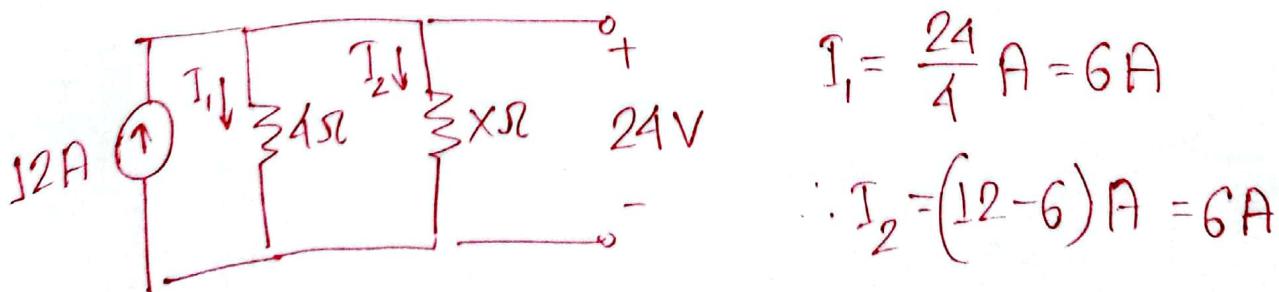At point $(24, 0)$, the circuit becomes —




$$I_1 = \frac{24}{4} A = 6 A$$

$$\therefore I_2 = (12 - 6) A = 6 A$$

$$\therefore x \cdot 6 = 24$$

$$\Rightarrow x = 4\Omega$$

4(c) Set B

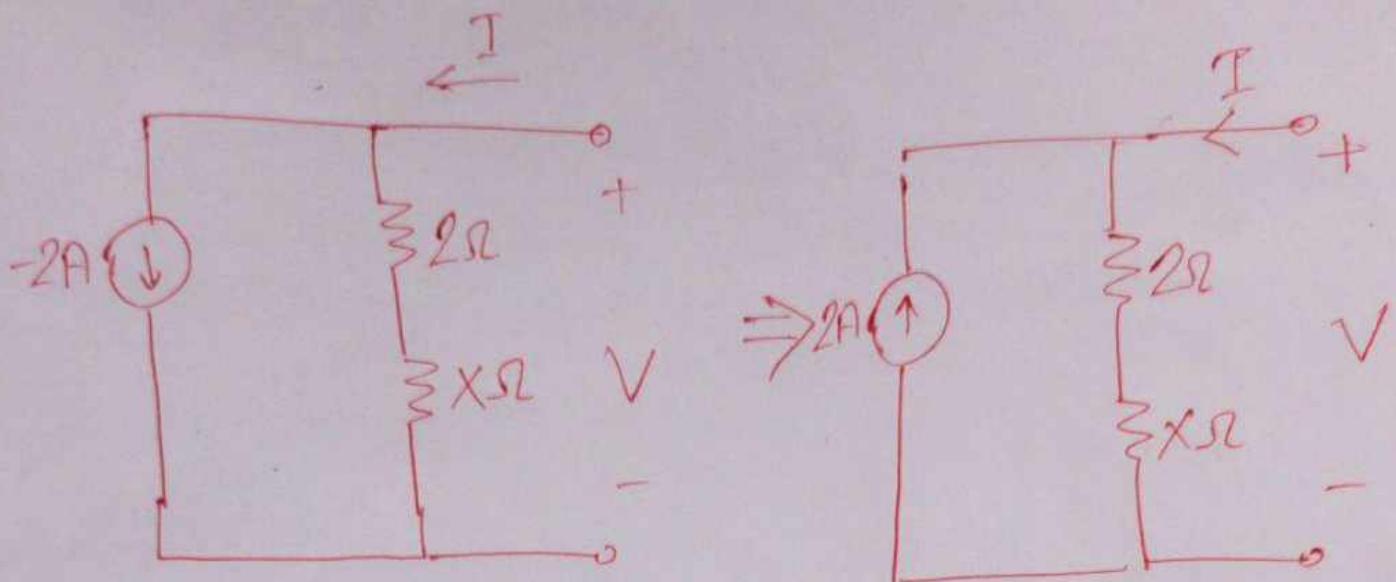

at point $(16, 0)$ of the I - V graph, the ckt becomes —

