
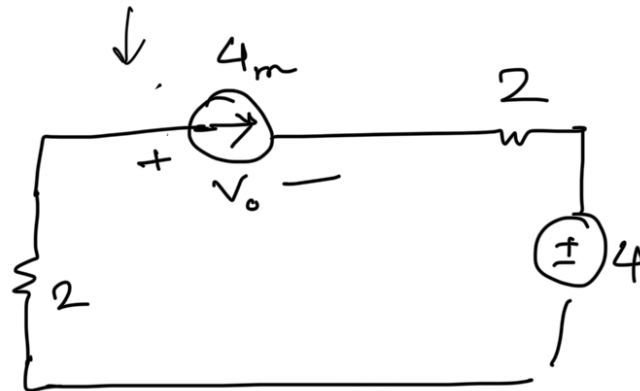


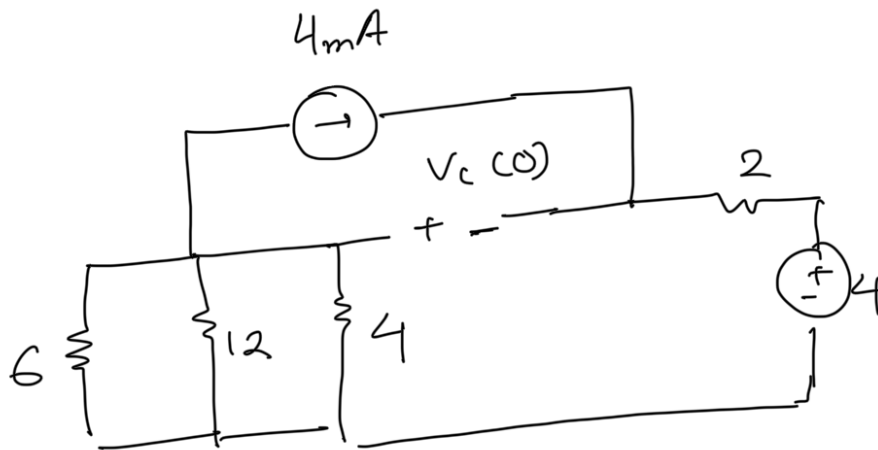

SFTB

①




②

[3]

$$V_c(\infty) = -2 \times 4 - 4 - 2 \times 4 = -20 \text{ V}$$

③

[3]

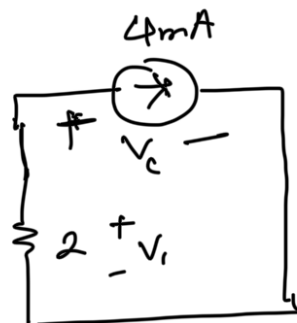

$$V_c(\infty) = -8 \text{ V}$$

$$S_0, \tau = 0.2 \text{ s}$$

④

$$R_{eq} = 2 \text{ k}\Omega$$

[3]

$$C_{eq} = 100 \mu F$$

$$S_o, \boxed{5\tau = 1s}$$

(d) for  $t < 0$   $\boxed{V_c(t) = 4V}$

[3]

for  $t > 0$   $V_c(t) = -8 + (-20 + 8)e^{-t/0.2}$

$$\boxed{= -8 - 12e^{-t/0.2}}$$

(e)  $\boxed{I_c(t) = 0 \text{ for } t < 0}$


[2]

$$I_c(t) = 100 \times 10^{-6} (-12e^{-t/0.2}) \times \left(-\frac{1}{0.2}\right)$$

$$\boxed{I_c(t) = 6 \times 10^{-3} e^{-t/0.2}}$$


(f)

[3]

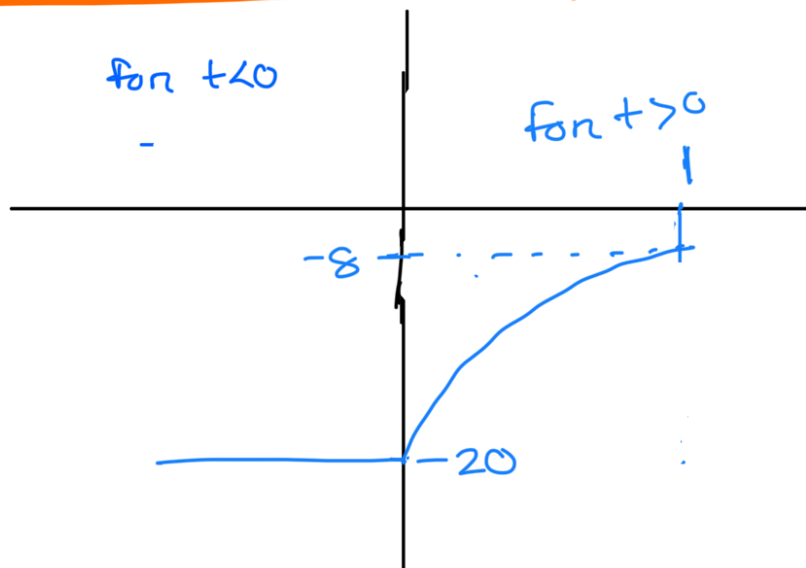

g

[3]

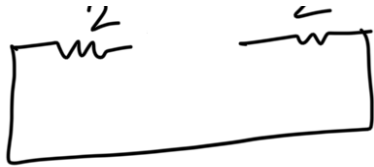

$$R_{eq} = 4k$$


$$C_{eq} = 100\mu F$$

$$\tau = 0.4s$$

$$\therefore 5\tau = 2s$$

Ques 2:

Q [7]

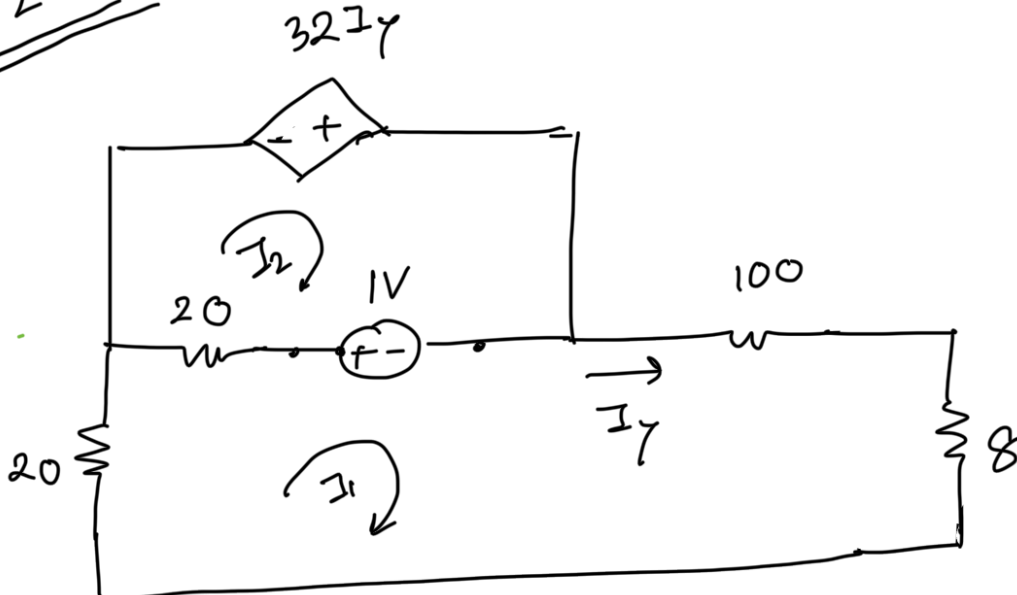

$$148I_1 - 20I_2 + 120$$

$$I_7 = I_1$$

$$148I_1 - 20I_2 = -1$$

$$20I_2 - 20I_1 - 1 - 32I_7 = 0$$

$$20I_2 - 20I_1 - 1 - 32I_1 = 0$$


$$-52I_1 + 20I_2 = 1$$

$$I_1 = 0, I_2 = \frac{1}{20}$$

$$R_{th} = \frac{1}{I_2 - I_1} = 20 \Omega$$

⑥ [8]

$V_{th}$

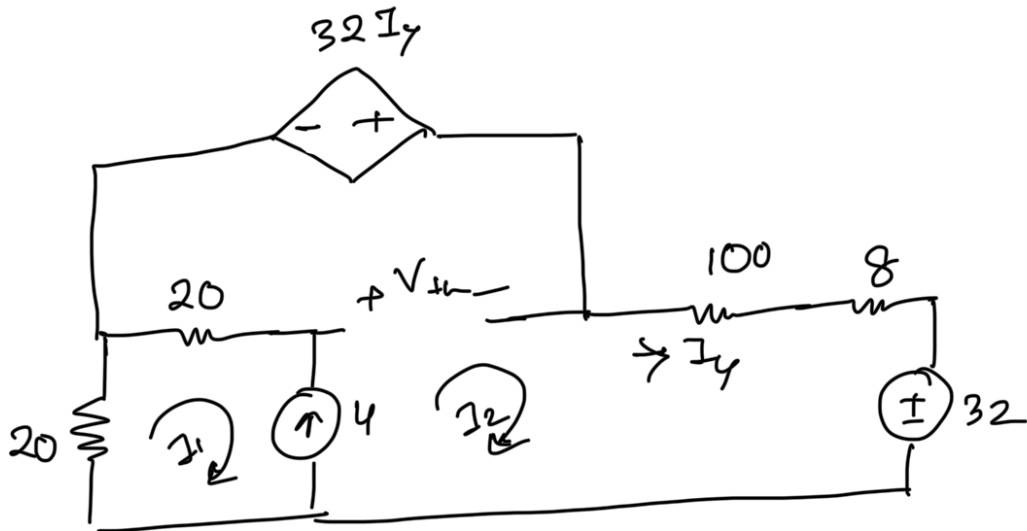

$$I_y = I_2$$

$$I_2 - I_1 = 4$$

$$20I_1 - 32I_y + 108I_2 + 32 = 0$$

$$20I_1 - 32I_2 + 108I_2 = -32$$

$$20I_1 + 76I_2 = -32$$

$$I_1 = -3.5 \text{ mA}, \quad I_2 = 0.5 \text{ mA}$$

$$-32I_y - V_{th} + 20(I_2 - I_1) = 0$$

$$\therefore V_{th} = -32I_2 + 20(I_2 - I_1)$$

$$V_{th} = 64V$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{64^2}{4 \times 20}$$

$$P_{max} = 51.2 \text{ W}$$

Ques 3:

①

[4]

$$\frac{4 \times 10^3}{4 \times 10^3 + 2} \times \angle 55 = 3 \angle 125.5$$

$$\begin{aligned} Z &= 5.682 - 11311.698j \\ &= 11311.7 \angle -89.97^\circ \Omega \end{aligned}$$

[1]

$$\textcircled{ii} R, C$$

[1]


iii

$$\frac{1}{\omega C} = 11311.698$$

$$C = 1.77 \mu F$$



⑥ 15V active:

[14]

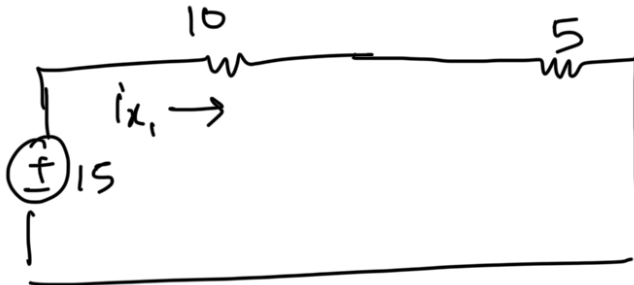

$$i_{x1} = \frac{15}{15} = 1$$

$2 \angle 30^\circ A$  active

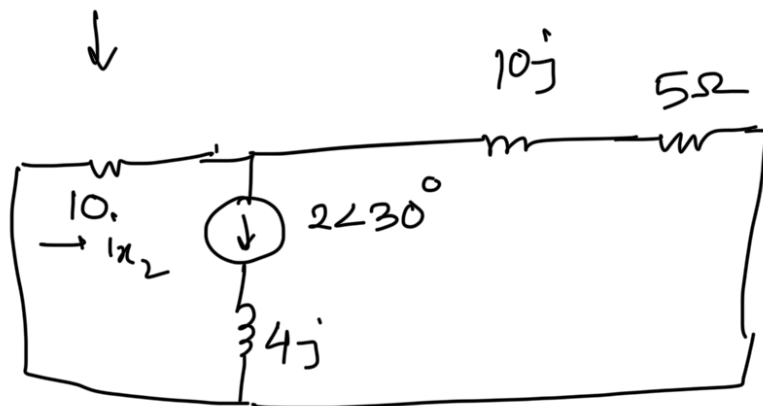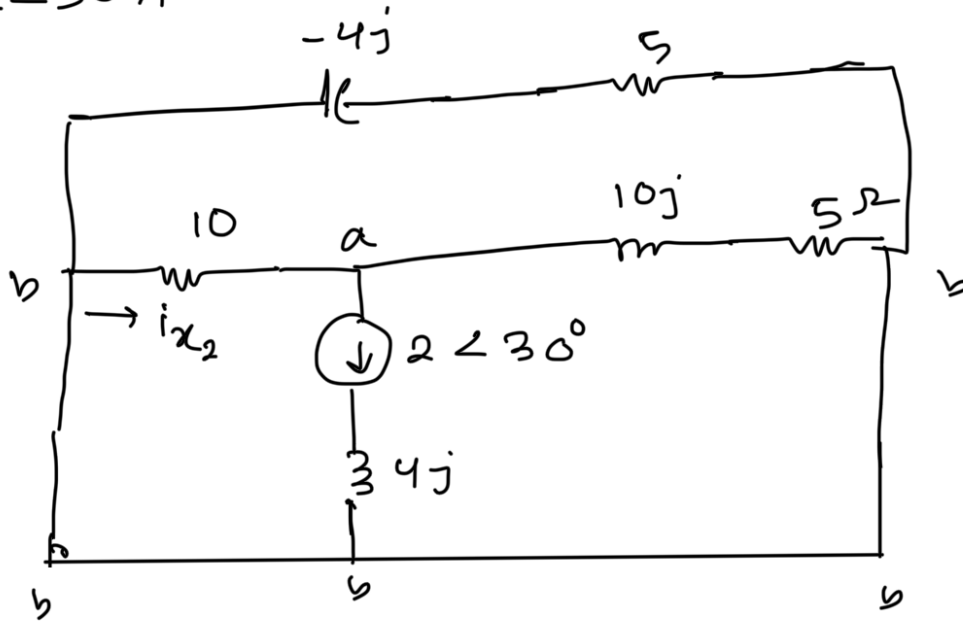


$$\therefore i_{x_2} = \frac{10^{-5}}{10^{-1} + (5 + 10j)^{-1}} \times 2 \angle 30^\circ$$

$$= 1.24 \angle 59.74^\circ$$

$$\therefore i_{x_2} = 1.24 \sin(2t + 59.74^\circ)$$

$5 \angle -45^\circ$  active:

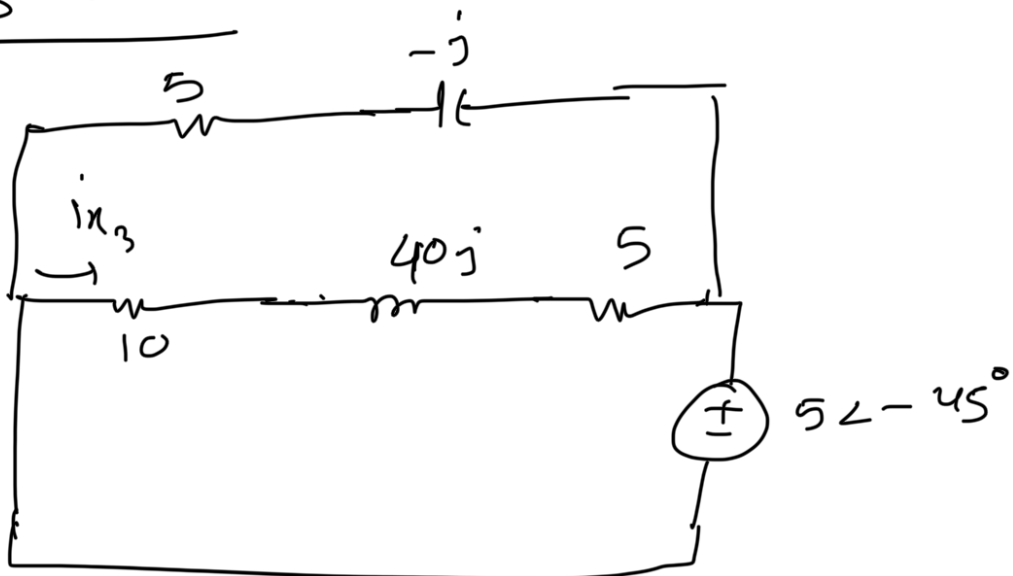

$$\text{So, } i_{x_3} = - \frac{5 \angle -45^\circ}{10 + 40j + 5}$$

$$= 0.11 \angle -114.44^\circ$$

$$i_{x_3} = 0.11 \cos(2t - 114.44^\circ)$$

$$\text{So, } i_x = i_{x_1} + i_{x_2} + i_{x_3}$$

$$\Rightarrow 1 + 1.24 \sin(2t + 59.74^\circ) \\ + 0.11 \cos(6t - 114.44^\circ)$$