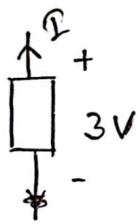


set B

① ②



$$P = -IV$$

$$\Rightarrow -12 = -I \times 3$$

$$I = 4 \text{ A}$$

⑥



$$4 + I_x = 2$$

$$I_x = -2 \text{ A}$$

$$\textcircled{c} +V_x - (2 \times 2) + 9 + 3 = 0$$

$$V_x = -8 \text{ V}$$

② ② Using nodal ,

$$\frac{V_1}{10} = \frac{V_1 - 20}{10}$$

$$V_1, V_2 : \frac{V_1 - 20}{10} + \frac{V_1 - V_3 - 20}{5} + 3 = V_y$$

$$(V_y = V_3)$$

$$\Rightarrow \frac{3}{10} V_1 - \frac{V_2}{5} - \frac{6}{5} V_3 = 3 - \textcircled{i}$$

$$\underline{V_3} : \frac{V_3}{10} + \frac{V_3 - V_1 + 20}{5} = 3$$

$$\Rightarrow -\frac{1}{5} V_1 + \frac{3}{10} V_3 = -1 - \textcircled{ii}$$

$$V_1 - V_2 = 18 - \textcircled{iii}$$


solving ①, ②, ③

$$V_1 = \frac{94}{5} = 18.8$$


$$V_2 = \frac{4}{5} = 0.8$$

$$V_3 = \frac{46}{5} = 9.2 = V_y - 2 = V_y$$

①

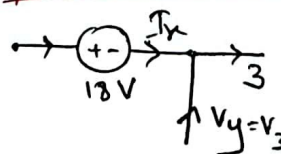

②

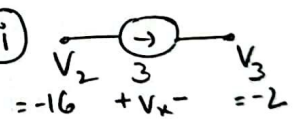

$$I_x + V_y = 3$$

$$V_x = -16 + 2 = -14$$

$$I_x = 3 - 9.2 = -6.2 \text{ A}$$

$$P = +IV$$

$$= + \left( \frac{5}{6.2} \right) \times 18$$

$$= +90 \text{ W}$$

$$= +90 \text{ W (absorbing)}$$

$$= 3 \times -14$$

$$= -42 \text{ W}$$

$$\text{(supplying)}$$

② Using mesh,

$$\underline{1,2,3} : -20 + 10i_1 + 5i_2 + 20 + 10i_3 = 0$$

$$10i_1 + 5i_2 + 10i_3 = 0 \quad \text{--- (i)}$$

$$i_3 - i_2 = 2 \quad \text{--- (ii)}$$


$$i_3 - i_1 = V_y \quad [V_y = 10i_3]$$

$$i_1 + 9i_3 = 0 \quad \text{--- (iii)}$$

solving,

$$\begin{aligned} i_1 &= 1.8 \\ i_2 &= -3.2 \\ i_3 &= -0.2 \end{aligned} \quad \text{mA}$$

$$V_y = -2 \quad (=V_3)$$

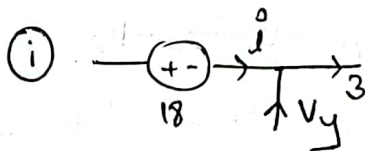

$$i + V_y = 3$$

$$i = 5$$

$$P = +IV$$


$$= +5 \times 18$$

$$= 90 \text{ W (absorbing)}$$

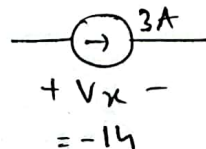(ii) consider mesh 1, 3 -

$$-20 + 10i_1 + 18 + V_x + V_y = 0$$

$$\begin{aligned} V_x &= 20 - 10(1.8) - 18 - (-2) \\ &= -14 \text{ V} \end{aligned}$$



$$\begin{aligned} +V_x - \\ &= -14 \end{aligned}$$

$$P = +IV$$

$$= +3 \times -14$$

$$= -42 \text{ W (supplying)}$$

②⑥ mesh:  $10i_1 + 5i_2 + 10i_3 = 0$  — (i)

$$i_3 - i_2 = 5 \text{ — (ii)}$$

$$i_1 + 9i_3 = 0 \text{ — (iii)}$$







$$(V_y = i_3 - i_1)$$

nodal:  $\frac{3}{10}V_1 - \frac{6}{5}V_3 = 3$  /  $3V_1 - 12V_3 = 30$  — (i)

$$-\frac{1}{5}V_1 + \frac{3}{10}V_3 = -1 \text{ / } -2V_1 + 3V_3 = -10 \text{ — (ii)}$$

$$V_1 - V_2 = 18 \text{ — (iii)}$$



$$(V_y = V_3)$$

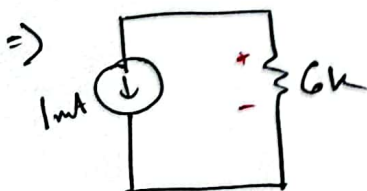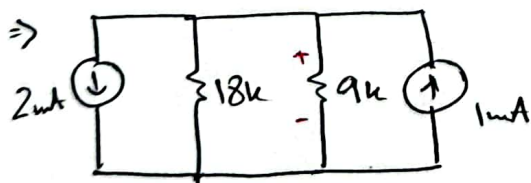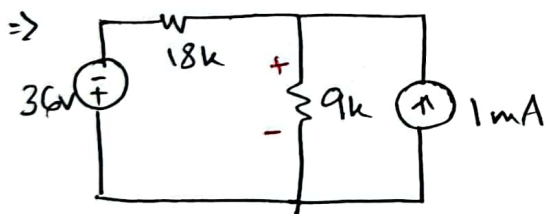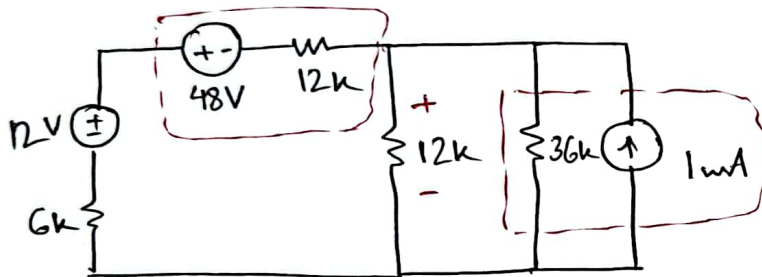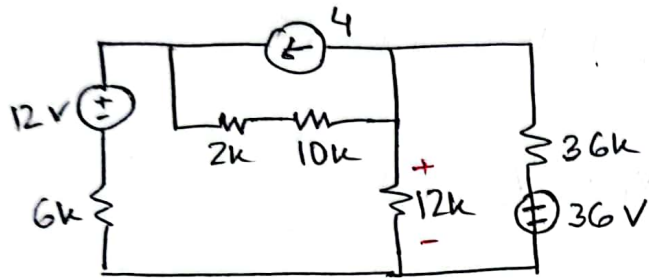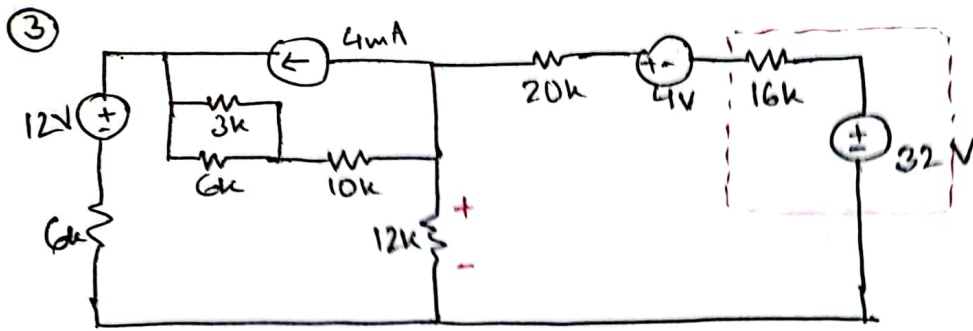

$$V_x = -1 \times 6$$

$$= -6V$$

4

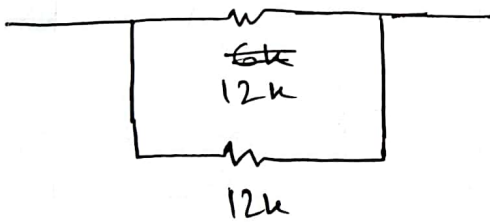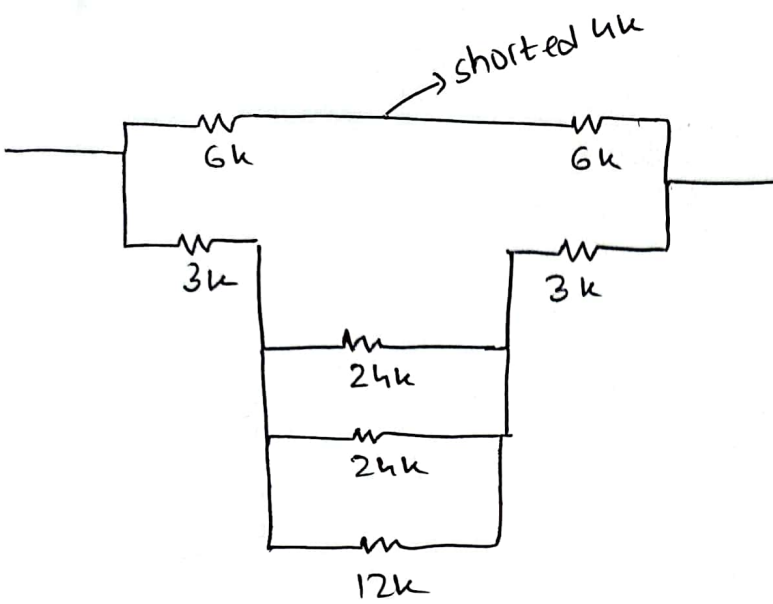

$$R_{eq} = 12k \parallel 12k$$

$$= 6k$$