

Q1:

(a) From the given circuit, $V_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$. When $V_L = 12$ V, $R_L = 1$ k Ω . So,

$$12 = \frac{1}{1 + R_{Th}} V_{Th} \quad (1)$$

When $V_L = 20$ V, $R_L = 2$ k Ω . So,

$$20 = \frac{2}{2 + R_{Th}} V_{Th} \quad (2)$$

Dividing the two equations 1 & 2,

$$\frac{6}{5} = \frac{2 + R_{Th}}{1 + R_{Th}} \Rightarrow R_{Th} = 4 \text{ k}\Omega$$

Substituting this to 1, $V_{Th} = 60$ V

Ans: 60 V, 4 k Ω

Alternate Solution using Max Power Transfer:

R_L	V_L	P_L
1 k Ω	12 V	144 mW
2 k Ω	20 V	200 mW
4 k Ω	30 V	225 mW
6 k Ω	36 V	216 mW
16 k Ω	48 V	144 mW
56 k Ω	56 V	56 mW

Thus, $P_{max} = 225$ mW, when $R_L = 4$ k Ω . $\therefore R_{Th} = 4$ k Ω . And since voltage across both the resistors will be same, $V_{Th} = 2 \times V_L = 60$ V.

(b) **Thevenin's theorem:** W.r.t. the ground given in the question, $V_b = 20$ V. Voltage of the +ve node of 10 V source = $20 - V_x$. Applying KCL to this node:

$$\frac{(20 - V_x) - 20}{5} + \frac{20 - V_x}{10} + \frac{20 - V_x - V_a}{10} + \frac{20 - V_x - V_x - V_a}{10} - 4 = 0$$

KCL at V_a ,

$$\frac{V_a - (20 - V_x)}{10} + \frac{V_a - (20 - V_x - V_x)}{10} = 0$$

Solving, $V_a = 30$ V. $\therefore V_{Th} = V_a - V_b = 30 - 20 = 10$ V.

Norton's theorem: Shorting a & b and w.r.t. the ground given, $V_a = V_b = 20$ V. Again KCL at $20 - V_x$ node,


$$\frac{20 - V_x - 20}{5} + \frac{20 - V_x}{10} + \frac{20 - V_x - 20}{10} + \frac{20 - V_x - V_x - 20}{10} - 4 = 0$$

Solving, $V_x = \frac{-10}{3}$ V. KCL at V_a ,

$$\frac{V_a - (20 - V_x)}{10} + \frac{V_a + V_x - (20 - V_x)}{10} + I_N = 0$$

Substituting values of V_a & V_x , $I_N = 1$ A

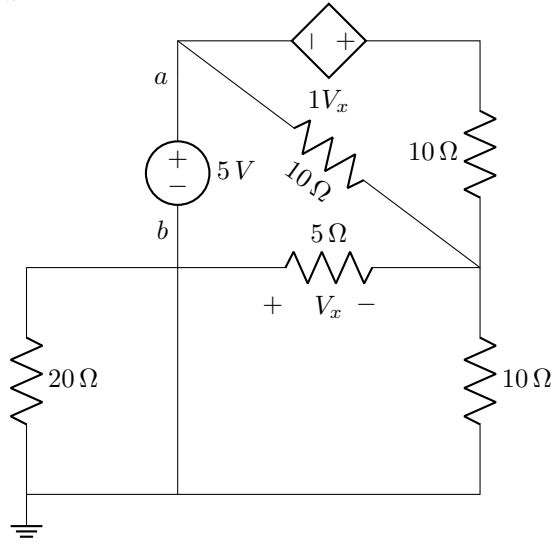R_{Th} : Turning off all independent sources, the reduced circuit looks like the following, with a dummy source of 5 V inserted between a-b terminals for finding R_{Th} .



$20\ \Omega$ is shorted. $V_b = 0$ V, $V_a = 5$ V. Applying KCL at $-V_x$ node,

$$\frac{-V_x}{5} + \frac{-V_x}{10} + \frac{-V_x - 5}{10} + \frac{-V_x - V_x - 5}{10} = 0$$

Solving, $V_x = -\frac{5}{3}$ V. KCL at V_a ,

$$\frac{V_a - (-V_x)}{10} + \frac{V_a + V_x - (-V_x)}{10} - I_{5V} = 0$$

Substituting values of V_a & V_x , $I_{5V} = \frac{1}{2}$ A. Now, $R_{Th} = \frac{5}{I_{5V}} = \frac{5}{\frac{1}{2}} = 10\ \Omega$.

$$\therefore P_{max} = \frac{V_{Th}^2}{4 \times R_{Th}} = \frac{I_N^2 \times R_N}{4} = \frac{V_{Th} \times I_N}{4} = 2.5\ W$$

Ans: 2.5 W

Q2: (a)

i. $5\tau = 5 \Rightarrow \tau = 1\ ms$

ii. $V_c(t) = V_f + [V_0 - V_f]e^{-\frac{t-t_i}{\tau}} = 6 + [2 - 6]e^{-\frac{t-0}{1 \times 10^{-3}}}$


iii. $R_{Th} = \frac{\tau}{C} = \frac{1 \times 10^{-3}}{1 \times 10^{-6}} = 1 \text{ k}\Omega$

$$R \parallel 2 \text{ k}\Omega = R_{Th} \Rightarrow R = 2 \text{ k}\Omega$$

Ans: $\tau = 1 \text{ ms}$, $V_c(t) = 6 - 4e^{\frac{-t}{1 \times 10^{-3}}}$, $R = 2 \text{ k}\Omega$


(b)

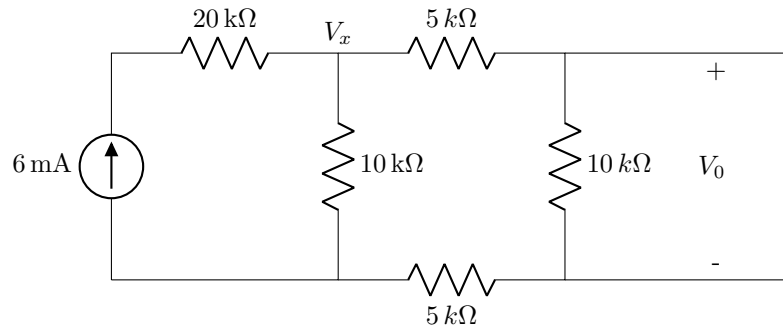i. Open circuit voltage at the terminals of the capacitor for $t < 0$, V_0 :



Using current divider, $I_{(5+10+5) \text{ k}\Omega} = \frac{10}{10+20} \times 6 = 2 \text{ mA}$. $\therefore V_0 = 2 \times 10 = 20 \text{ V}$.

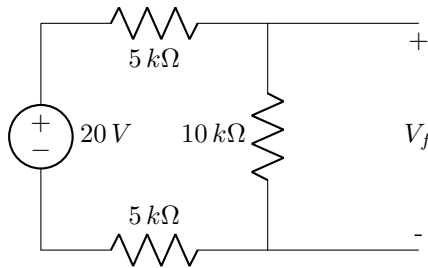
Open circuit voltage at the terminals of the capacitor for $t > 0$, V_f :



Using voltage divider, $V_f = \frac{10}{5+10+5} \times 20 = 10 \text{ V}$

Ans: $V_0 = 20 \text{ V}$, $V_f = 10 \text{ V}$

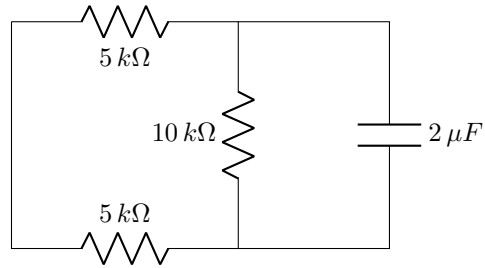ii. For $t > 0$, killing all the independent sources:



$$\therefore R_{Th} = (5 + 5) \parallel 10 = 5 \text{ k}\Omega.$$


$$\therefore \tau = R_{Th} \times C = 5 \times 2 = 10 \text{ ms}.$$

$$\text{iii. } V(t) = 10 + [20 - 10]e^{-\frac{t}{10 \times 10^{-3}}}$$


$$\text{iv. } i(t) = C \frac{dV_c}{dt} = 2 \times 10^{-6} \times \frac{-1}{10 \times 10^{-3}} \times (10e^{-\frac{t}{10 \times 10^{-3}}}) = -2e^{-\frac{1}{10 \times 10^{-3}}} \text{ mA}$$

$$\text{v. Using voltage divider, } V_R(t) = \frac{6}{4+6} \times V(t) = 6 + 6e^{-\frac{1}{10 \times 10^{-3}}}$$

Q3: Using source transformation:

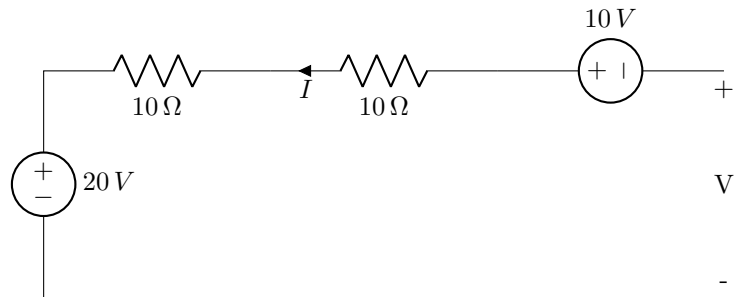

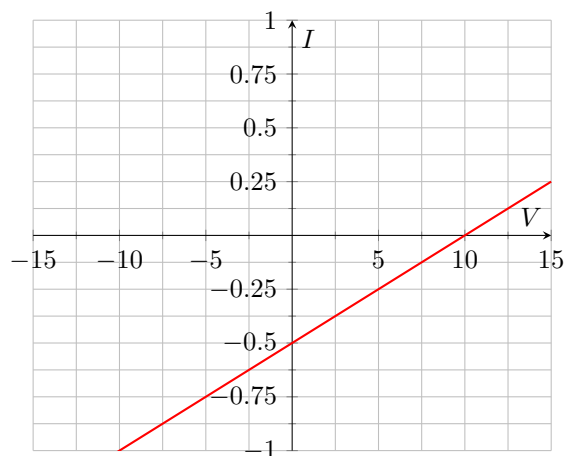Applying KVL in the loop, $-20 - 10I - 10I + 10 + V = 0 \Rightarrow I = \frac{V}{20} - \frac{1}{2}$



Q4: (a)

$$-16\sin(150\pi t + 45^\circ) = 16\cos(150\pi t + 45^\circ + 90^\circ) = 16\cos(150\pi t + 135^\circ)$$

$$\therefore \Delta\phi = 135^\circ \equiv \frac{T}{360^\circ} \times 135^\circ = \frac{2\pi}{150\pi} \times \frac{3}{8} = \frac{1}{200} \text{ s} = 5 \text{ ms}$$

Ans: 5 ms shifted to the left

(b) $T = 72 - 8 = 64 \text{ ms}$. Let the initial phases be ϕ_1 and ϕ_2 , respectively.

$$\phi_1 = (16 - 8) \times 10^{-3} \times \frac{360000^\circ}{64} = 45^\circ$$

$$\phi_2 = (0 - 16) \times 10^{-3} \times \frac{360000^\circ}{64} = -90^\circ$$

$$\therefore v_1(t) = 32\cos\left(\frac{360000}{T}t + \phi_1\right) = 32\cos\left(\frac{360000}{64}t + 45^\circ\right)$$

$$\therefore v_2(t) = 16\sin\left(\frac{360000}{64}t - 90^\circ\right) = -16\cos\left(\frac{360000}{64}t\right) = 16\cos\left(\frac{360000}{64}t + 180^\circ\right)$$

i. $\Delta\phi = 180^\circ - 45^\circ = 135^\circ$. $v_2(t)$ is leading.

ii. $v_1(t) = 32\cos\left(\frac{360000}{64}t + 45^\circ\right)$

$$v_2(t) = 16\cos\left(\frac{360000}{64}t + 180^\circ\right)$$