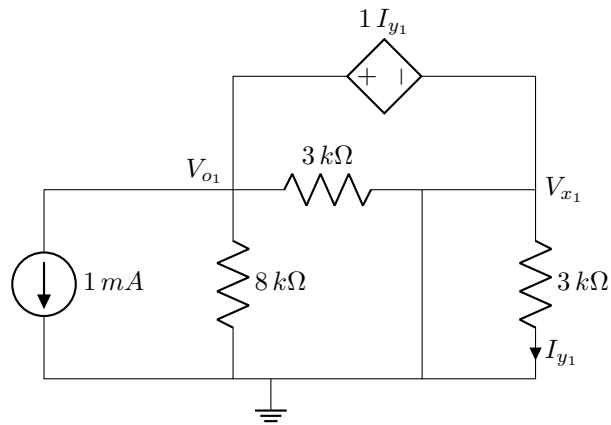


Question 1:


When **1 mA** active:



$$V_{x_1} = 0$$

$$\therefore V_{o1} = 1 \times I_{y1} = 1 \times \frac{V_{x_1}}{3} = 0$$


When **8 V** is active:

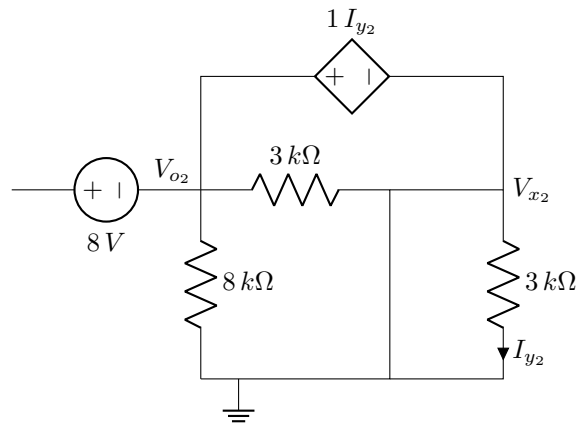

$$V_{x_2} = 0$$

$$\therefore V_{o2} = 1 \times I_{y2} = 1 \times \frac{V_{x_2}}{3} = 0$$

When **6 V** is active:

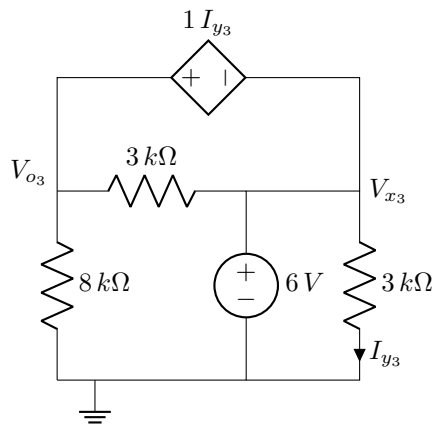

$$V_{x_3} = 6\text{ V}$$

$$V_{o_3} = V_{x_3} + 1 \times \frac{6}{3} = 8\text{ V}$$

$$\therefore V_o = V_{o_1} + V_{o_2} + V_{o_3} = 8\text{ V}$$


Question 2:

Circuit 1: KCL at 'V' node,

$$I = 2 + \frac{V - 8}{2}$$

$$\Rightarrow I = \frac{V}{2} - 2$$

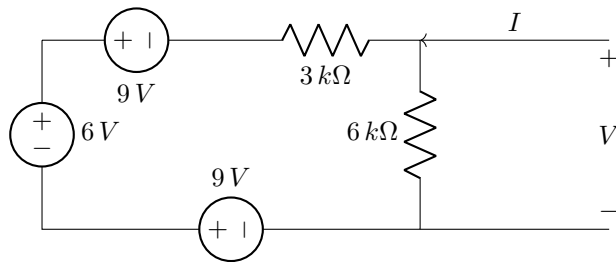Circuit 2: Source transformed & reduced circuit:



KVL in the left loop (let loop current I_1),

$$-6 + 9 + 3I_1 + 6(I_1 + I) - 9 = 0$$

KCL at 'V',

$$I_1 = \frac{V}{6} - I$$

So,

$$3 \left(\frac{V}{6} - I \right) + 6 \left(\frac{V}{6} - I + I \right) - 9 = -3$$

$$\Rightarrow I = \frac{V}{2} - 2$$

Question 3:

(a) For $t < 0$:

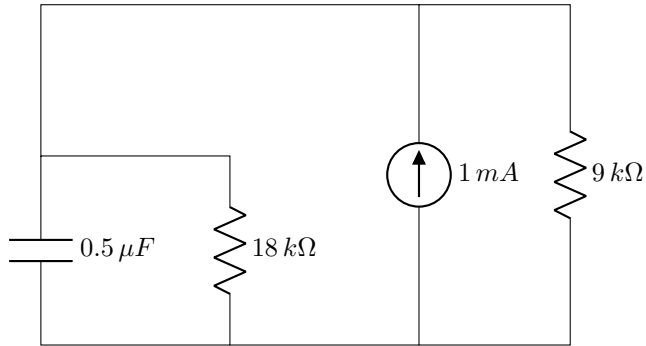


Figure 1: $t < 0$

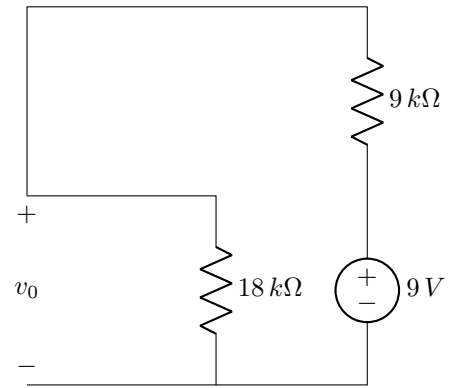


Figure 2: Reduced circuit

$$\therefore v_o = 9 \times \frac{18}{18 + 9} = 6 \text{ V}$$

For $t > 0$:

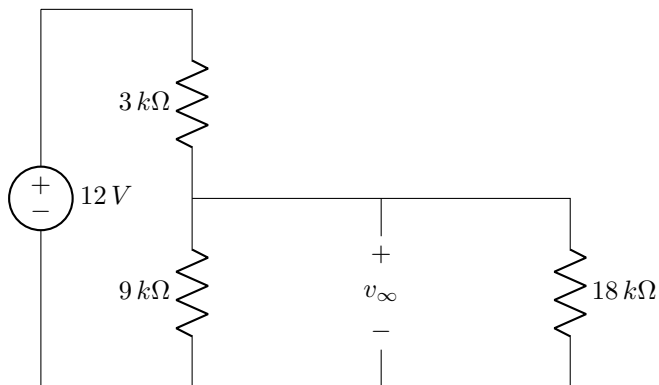


Figure 3: $t > 0$

$$\tau = 0.5 \times (3 || 9) || 18 = 1 \text{ ms}$$

$$\therefore v_{\infty} = 12 \times \frac{9 || 18}{3 + (9 || 18)} = 8 \text{ V}$$

(i) $\therefore v(t) = v_{\infty} + [v_0 - v_{\infty}]e^{-\frac{t-0}{1}} = 8 + [6 - 8]e^{-\frac{t}{1}} = 8 - 2e^{-t} V$, where t is in ms.

(ii) $i(t) = C \frac{dv(t)}{dt} = 0.5 \times \left(-\frac{1}{1}\right) \times -2e^{-t} = 1e^{-t} mA$, where t is in ms.

(iii) Energy gained by the capacitor $= \frac{1}{2} \times 0.5[6^2 - 8^2] = 7 \mu J$

(b) (i) Transient duration $= 5\tau = 15 ms$

(ii) Voltage after switching $= v_{\infty} = -12 V$

Voltage before switching $= v_0 = -12 - 4 = -16 V$


(iii) Opening the capacitor to find v_{∞} ,

$$v_{\infty} = -\frac{R}{4+R} \times 16 = -12 \Rightarrow R = 12$$

$$\therefore C = \frac{3}{12||4} = 1.0 \mu F$$

Question 4:

V_{Th} :

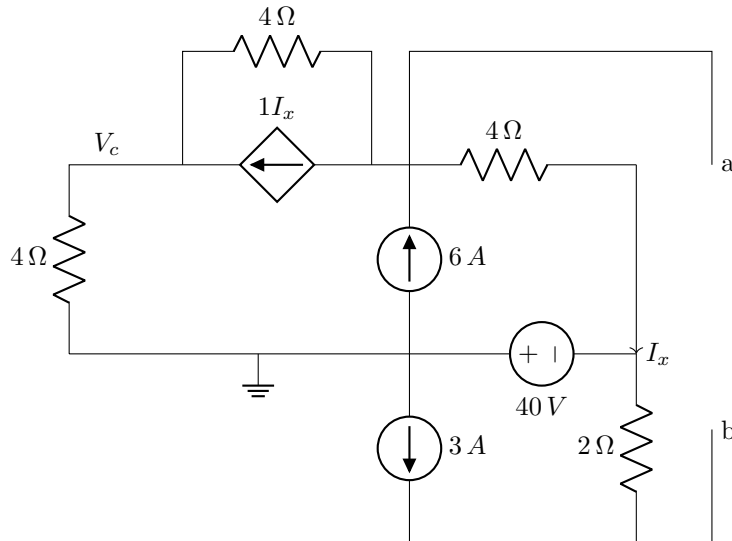

KCL at 'b',

$$-3 + \frac{V_b - (-40)}{2} = 0 \Rightarrow V_b = -34 V$$

KCL at 'a',

$$\frac{V_a - (-40)}{4} - 6 + 1 \times \frac{V_a - (-40)}{4} + \frac{V_a - V_c}{4} = 0$$


KCL at 'c',

$$1 \times \frac{V_a - (-40)}{4} + \frac{V_a - V_c}{4} = \frac{V_c - 0}{4}$$

Solving, $V_a = -18\text{ V}$, $V_c = 2\text{ V}$

$$\therefore V_{Th} = V_{ab} = V_a - V_b = 16\text{ V}$$

R_{Th} :

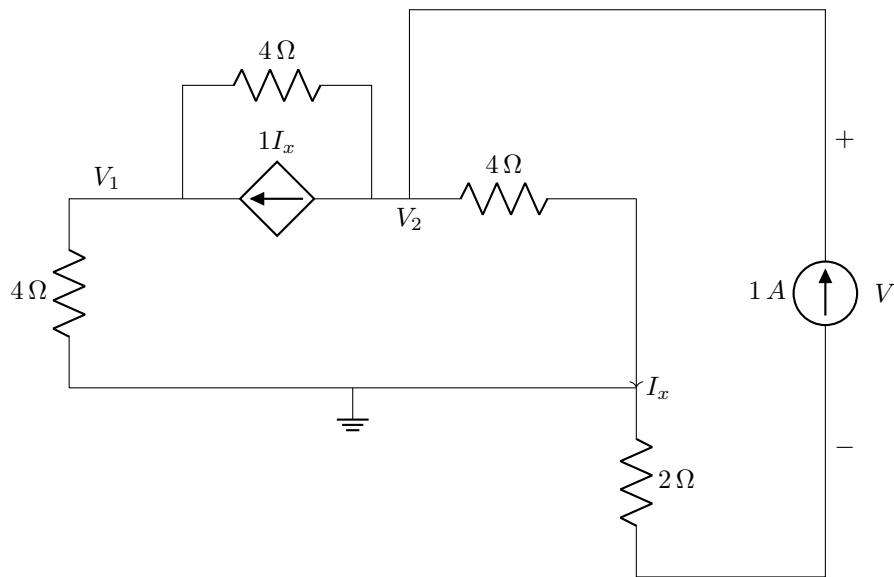

KCL at 'V1',

$$\frac{V_1 - 0}{4} + \frac{V_1 - V_2}{4} - 1 \times \frac{V_2 - 0}{4} = 0$$

KCL at 'V2',

$$\frac{V_2 - V_1}{4} + 1 \times \frac{V_2 - 0}{4} - 1 + \frac{V_2 - 0}{4} = 0$$

Solving, $V_1 = 2\text{ V}$, $V_2 = 2\text{ V}$. Now, applying KVL, we see,

$$-V_2 + V + (-1) \times 2 = 0$$

$$\Rightarrow V = 4\text{ V}$$

$$\therefore R_{Th} = \frac{V}{1} = 4\text{ }\Omega$$

$$\therefore P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{16^2}{4 \times 4} = 16\text{ W}$$