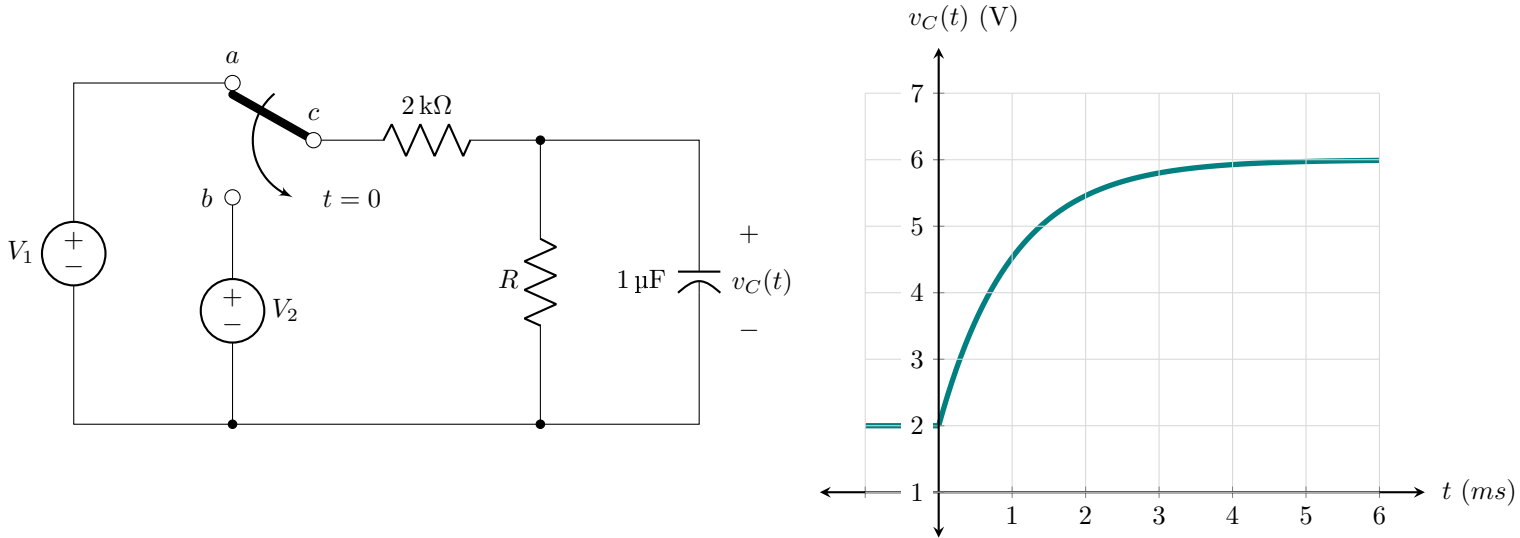



■ Question 2 of 4

[CO3] [25 marks]

- (a) The switch in the following circuit moves from position a to position b at time $t = 0$, while the terminal c remains fixed. As a result, the capacitor voltage $v_C(t)$ increases exponentially, as shown in the plot below with respect to time t .



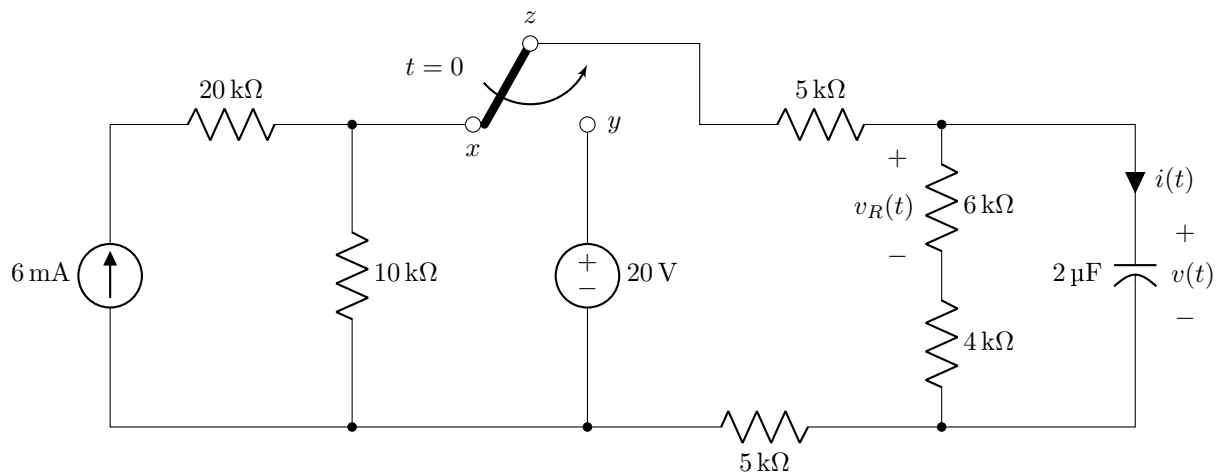- (i) [1 mark] What is the time constant of the RC circuit?
- (ii) [2 marks] Write an expression for the capacitor voltage $v_C(t)$ for $t > 0$ as a function of time.
- (iii) [3 marks] Based on the time constant determined in (i), determine the value of the resistance R in the circuit.
- (b) The switch in the following circuit moves from position x to position y at time $t = 0$, while the terminal z remains fixed.




Analyze the **Transient Behavior** of the RC circuit shown above to answer the following queries-

- (i) [7 marks] Determine the initial and final steady-state voltages of the capacitor, before and long after the switch is moved.
- (ii) [4 marks] Determine the time constant of the circuit.
- (iii) [2 marks] Using the values obtained in parts (i) and (ii), write the expression for the capacitor voltage $v(t)$ for $t > 0$ as a function of time.
- (iv) [3 marks] Determine the current $i(t)$ through the capacitor for $t > 0$ as a function of time.
- (v) [3 marks] Using the $v(t)$ from part (iii), determine the voltage $v_R(t)$ across the $6\text{ k}\Omega$ resistor for $t > 0$ as a function of time.

■ Question 3 of 4

[CO3] [10 marks]

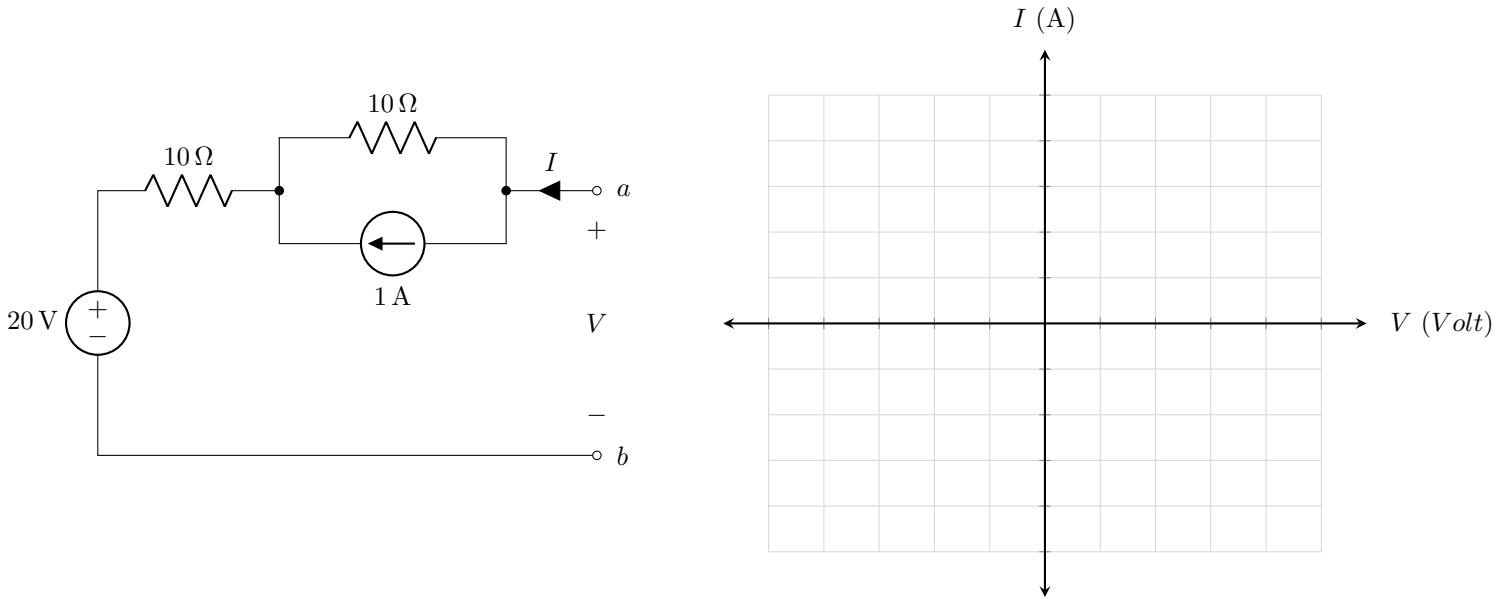
For the circuit shown below, derive the I - V characteristic equation with respect to terminals a and b , and plot it on the blank grid provided. Note that V and I are the only variables allowed in the equation; all other quantities must be constants. You must label the axes with appropriate values.



■ Question 4 of 4

[CO3] [10 marks]

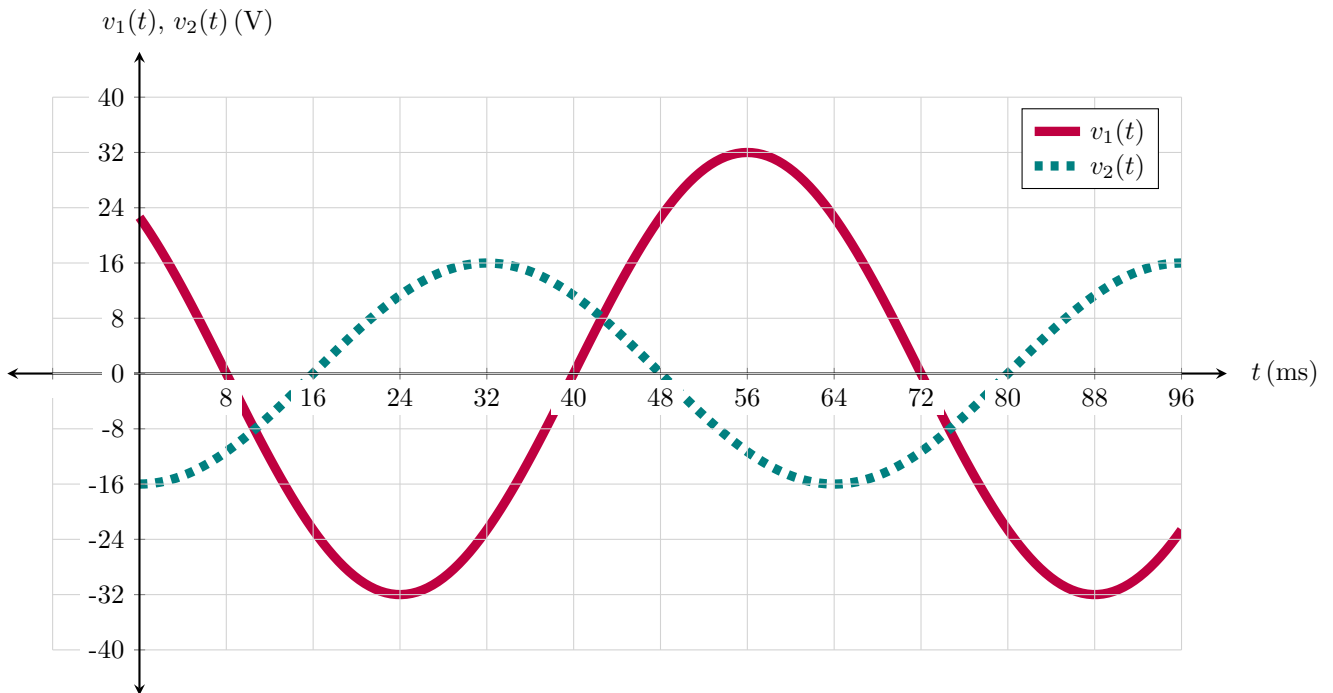- (a) [4 marks] By how much time in ms is the sinusoidal voltage $-16\sin(150\pi t + 45^\circ)$ V shifted to the left or right compared to the voltage $5\cos(150\pi t)$ V?
- (b) Two voltage waveforms $v_1(t)$ and $v_2(t)$ from an ac circuit are plotted below as a function of time t .



- (i) [3 marks] Determine the phase difference ($0^\circ \leq \Delta\varphi \leq 180^\circ$) between the two and identify which one is leading.
- (ii) [3 marks] Write analytical expressions for both $v_1(t)$ and $v_2(t)$ as a function of t with the initial phases (φ) in degrees, where $-180^\circ \leq \varphi \leq 180^\circ$.