

ID:

Name:

**Brac University**

Semester: Spring 2024

Course Code: CSE250

Circuits And Electronics

Set

B

Assessment: *Final Exam*

Duration: 1 hour 40 minutes

Date: May 10, 2025


Full Marks (incl. bonus 5): 55

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, both the **answer script** and the **question paper** must be returned to the invigilator.
- ✓ All **3 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Draw the plot associated with the question **1(f)** in the grid provided on the question paper.
- ✓ Symbols have their usual meanings.

■ Question 1 of 3


[CO3] [20 marks]

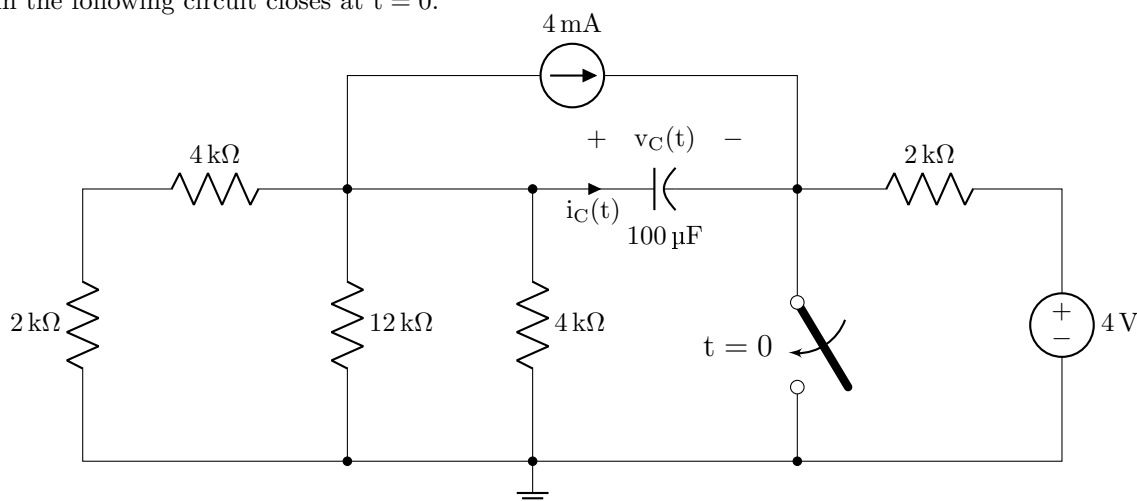The switch in the following circuit closes at $t = 0$.




Analyze the Transient Behavior to answer the following questions–

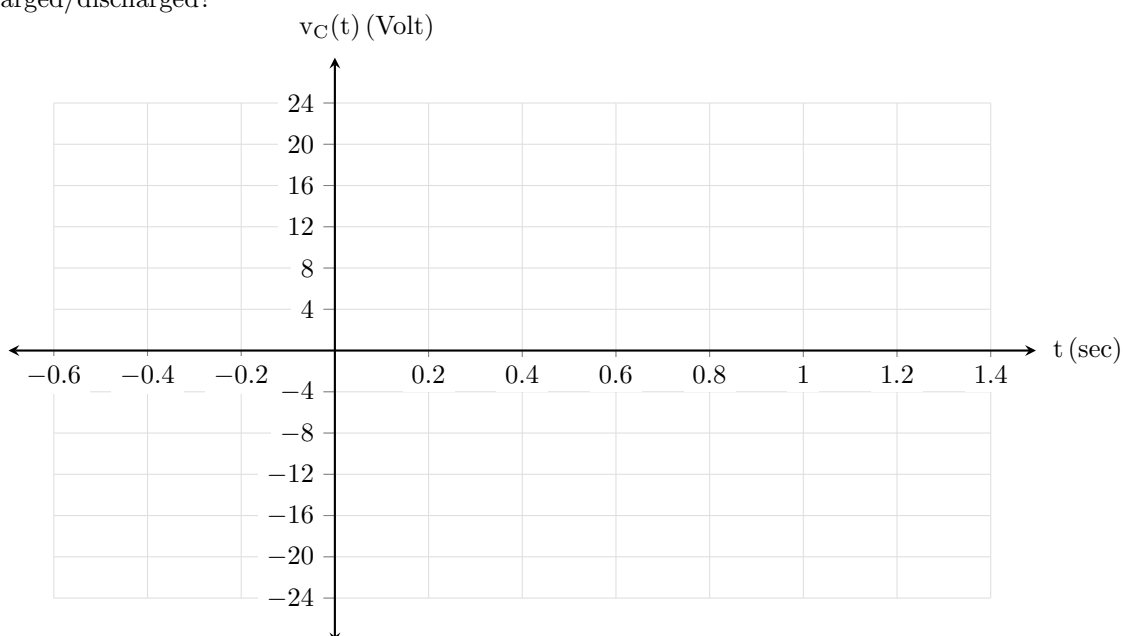- (a) [3 marks] Determine the voltage $v_C(0)$ across the capacitor before switching.
- (b) [3 marks] Determine the final stable voltage $v_C(\infty)$ across the capacitor after switching.
- (c) [3 marks] How much time is required for the capacitor voltage to reach steady-state from its initial value in (a)?
- (d) [3 marks] Write an expression of the voltage $v_C(t)$ as a function of time t for both $t < 0$ and $t \geq 0$.
- (e) [2 marks] Determine an expression of the capacitor current $i_C(t)$ as a function of time t for both $t < 0$ and $t \geq 0$.
- (f) [3 marks] Plot $v_C(t)$ found in (d) as a function of time t for both $t < 0$ and $t \geq 0$ on the grid provided below. Mark the time constant point on the curve.
- (g) [3 marks] If the arrow in the switch pointed in the opposite direction, how much time would the capacitor take to be fully charged/discharged?



■ Question 2 of 3

[CO2] [15 marks]

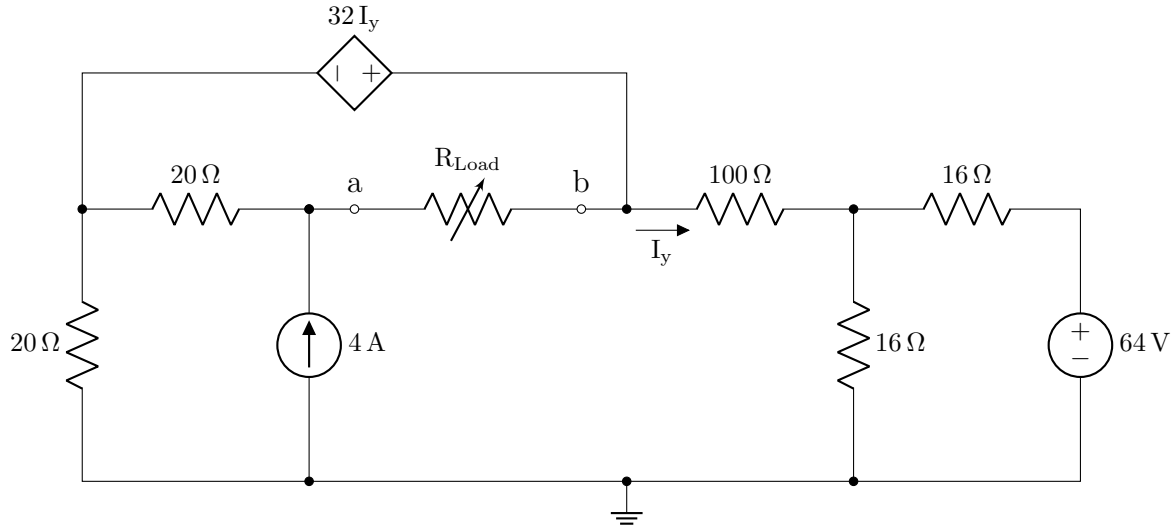

Apply Thevenin's/Norton's Theorem to answer the following queries–


(You may use any circuit theorem or technique to simplify the circuit.)

- [7 marks] Determine the value of R_{Load} connected between a and b so that the circuit delivers maximum power to it.
- [8 marks] Determine the value of the maximum power.

■ Question 3 of 3

[CO2] [20 marks]

- $z_{Unknown}$ in the following circuit is composed of one or more passive circuit elements. If the input voltage to the following circuit is $v_s(t) = 9 \cos(50t + 55^\circ)$ V and the voltage across the $4\text{ k}\Omega$ resistor is $v_o(t) = 3 \cos(50t + 125.5^\circ)$ V as labeled in the diagram,
 - [4 marks] Determine the impedance of $z_{Unknown}$.
 - [1 mark] What type of circuit element(s) (R and/or L and/or C) does $z_{Unknown}$ consist of?
 - [1 mark] Determine the value of the circuit element identified in (ii) with appropriate units.

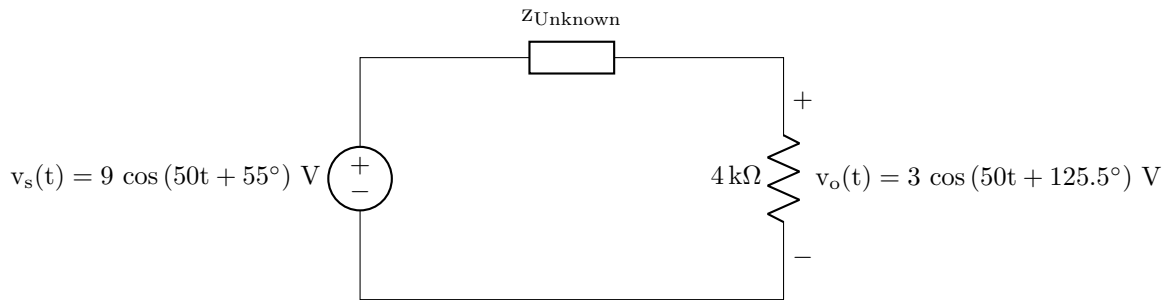

- [14 marks] For the circuit shown below, determine the current $i_x(t)$.

