


# Q-1(Node)

## Set B

Monday, 25 November, 2024

7:36 AM

(a)

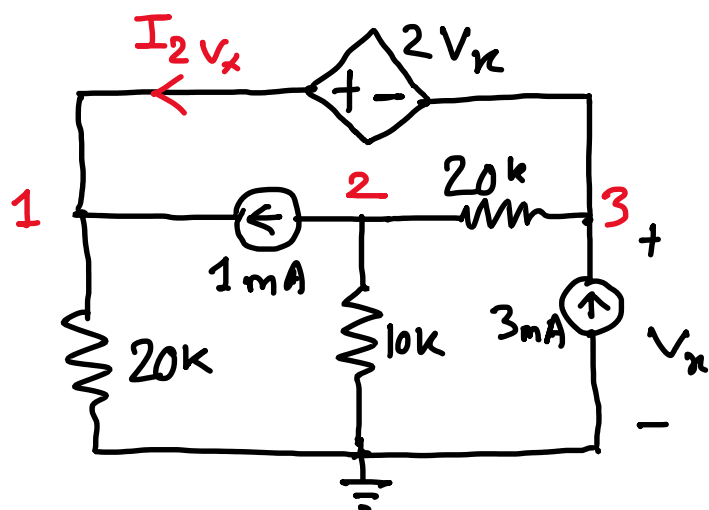

Supernode KCL (1 & 3) :

$$\frac{V_1}{20} + \frac{V_3 - V_2}{20} = 1 + 3$$

Supernode KVL :

$$V_1 - V_3 = 2V_x = 2V_3$$

$$\Rightarrow V_1 - 3V_3 = 0$$

KCL at '2' :

$$\frac{V_2}{10} + \frac{V_2 - V_3}{20} + 1 = 0$$

Solving,

$$V_1 = 60 \text{ V}$$

$$V_2 = 0 \text{ V}$$

$$V_3 = 20 \text{ V}$$

(b)

$$P_{2V_x} = -2V_x \times I_{2V_x}$$

$$= -(V_1 - V_3) \times \left[ \frac{V_1}{20} - 1 \right]$$

$$= -40 \times 2 = -80 \text{ mW}$$


(Supplying)

## Q-2(Mesh)

Monday, 25 November, 2024

7:20 AM

(a)

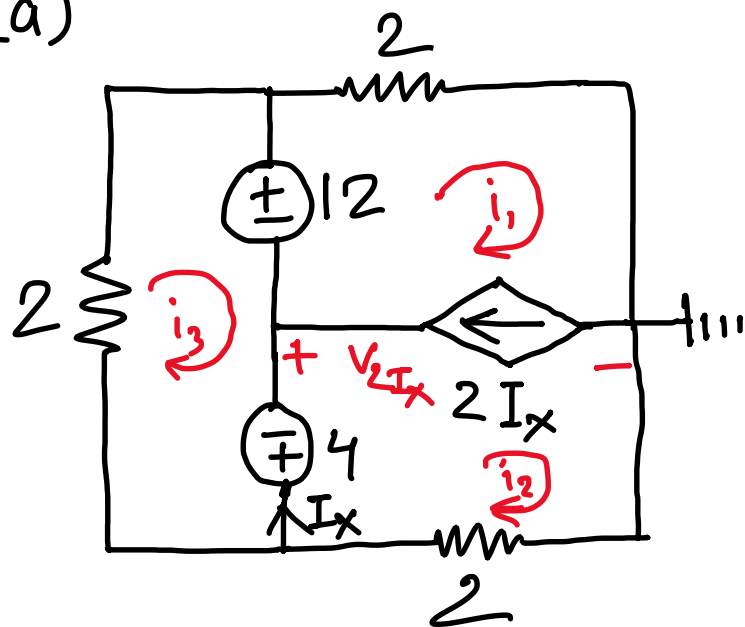

Supermesh KVL:

$$2i_1 + 4 + 2i_2 - 12 = 0$$

$$\Rightarrow i_1 + i_2 = 4$$

Supermesh KCL:

$$i_1 = 2I_x + i_2$$

$$\Rightarrow i_1 = 2(i_2 - i_3) + i_2$$

$$\Rightarrow i_1 - 3i_2 + 2i_3 = 0$$

Solving,

$$i_1 = 5 \text{ A}$$

$$i_2 = -1 \text{ A}$$

3rd mesh KVL:

$$2i_3 + 8 = 0$$

$$\Rightarrow i_3 = -4 \text{ A}$$

(b) KVL in mesh 2  $\Rightarrow 4 + 2i_2 + V_{2I_x} = 0$


$$\Rightarrow V_{2I_x} = -4 - 2 \times (-1) = -2 \text{ V}$$

## Q-2(Nodal)

Monday, 25 November, 2024

7:11 AM

(a)

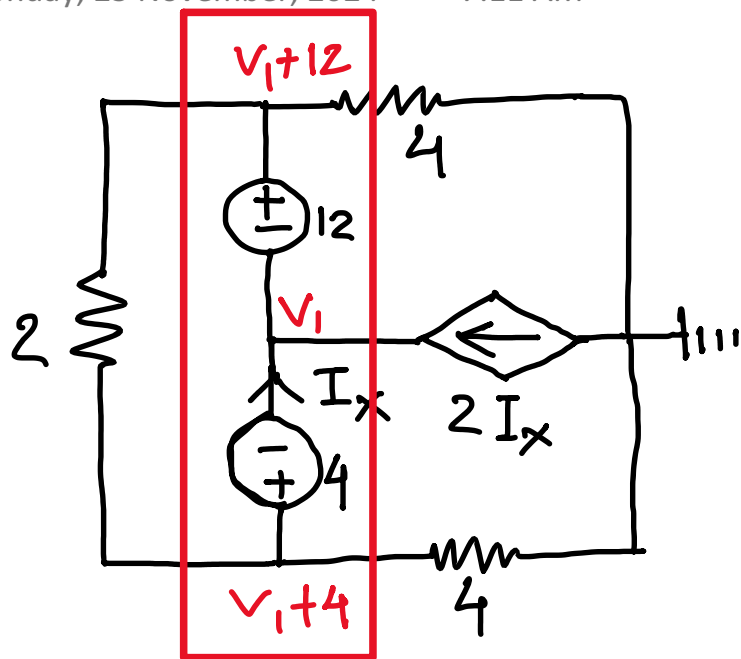

Supernode

KCL at  $V_1 + 8$ ,

$$\Rightarrow \frac{V_1 + 12 - (V_1 + 4)}{2} - \frac{V_1 + 4}{2} - I_x = 0$$

$$\Rightarrow I_x = 2 - \frac{V_1}{2}$$

KCL at supernode:

$$\frac{V_1 + 12}{2} + \frac{V_1 + 4}{2} - 2 \times \left(2 - \frac{V_1}{2}\right) = 0$$

$$\therefore V_1 = -2V$$

$\therefore$  Node voltages  $-2V$ ,  $2V$  &  $10V$ .

(b) Voltage of  $2I_x$  current source



$$= V_1 = -2V$$

Q-3

Monday, 25 November, 2024

7:51 AM

(a)

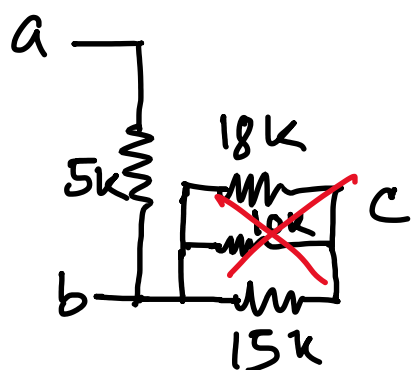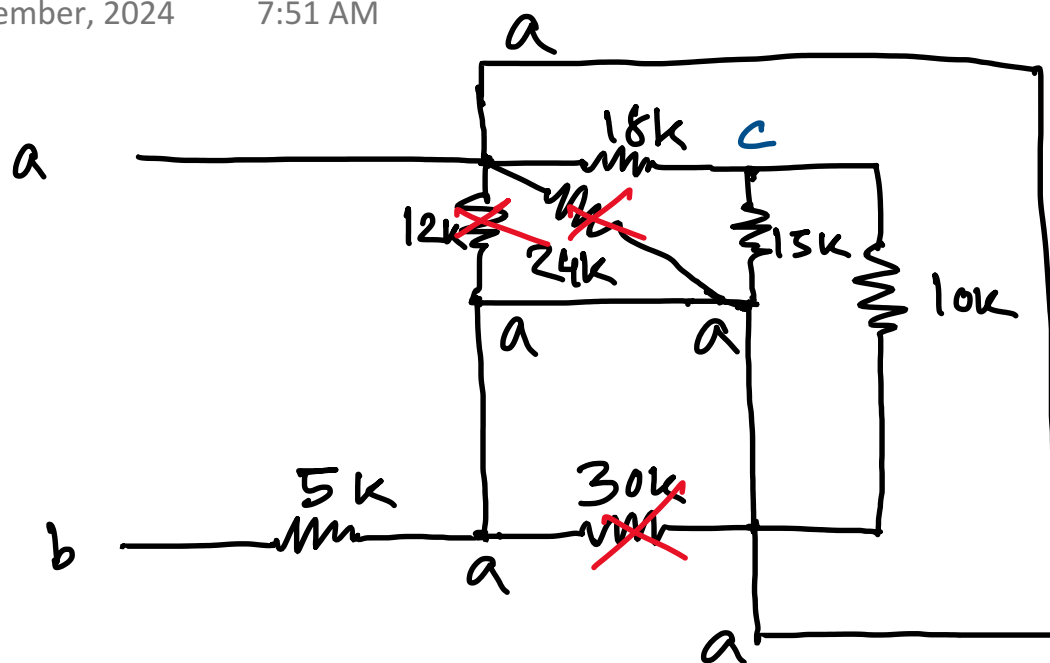

$$\therefore R_{ab} = 5k\Omega$$

$$(b)(i) \text{ KVL} \rightarrow -V_y + (-6) + 12 - 24 - (-4) + 8 + 12 = 0$$

$$\Rightarrow V_y = 6V$$

$$(ii) \text{ KVL} \rightarrow -V_{ab} - 24 - (-4) + 8 = 0$$

$$\Rightarrow V_{ab} = -12V$$